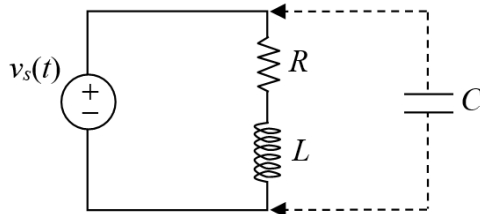


NCTU-ECE Introduction to Electric Circuit (C)

Practice Problems (2023/12/22)

60%

1. Consider the following circuit with the source  $v_s(t) = 5\cos(10t)$  connected by the payload  $R=10\Omega$  and  $L=0.1\text{H}$  in series.



- What is the complex power delivered by the source  $v_s(t)$ ?
- What is the average power dissipated by the payload?
- What is the power factor of the payload?
- Choose the capacitance  $C$  that will give a unity power factor?

40%

2. Determine the transfer function  $\hat{h}(s) = \frac{\hat{v}_o(s)}{\hat{v}_s(s)}$ .

