

Chap 1 Fundamental Concepts

1.1 SI Units and Prefixes

SI Units			
Quantity	Unit	Symbol	Derived unit
length	meter	m	
mass	kilogram	kg	
time	second	s	
current	ampere	A	
voltage	volt	V	$\text{kg} \cdot \text{m}^2 \cdot \text{A}^{-1} \cdot \text{s}^{-3}$
power	watt	W	$\text{kg} \cdot \text{m}^2 \cdot \text{s}^{-3}$
energy	joule	J	$\text{kg} \cdot \text{m}^2 \cdot \text{s}^{-2}$
charge	coulomb	C	$\text{A} \cdot \text{s}$
resistance	ohm	Ω	$\text{kg} \cdot \text{m}^2 \cdot \text{A}^{-2} \cdot \text{s}^{-3}$
conductance	siemens	S	$\text{A}^2 \cdot \text{s}^3 \cdot \text{kg}^{-1} \cdot \text{m}^{-2}$
capacitance	farad	F	$\text{A}^2 \cdot \text{s}^4 \cdot \text{kg}^{-1} \cdot \text{m}^{-2}$
inductance	henry	H	$\text{kg} \cdot \text{m}^2 \cdot \text{A}^{-2} \cdot \text{s}^{-2}$
requeency	hertz	Hz	s^{-1}

* 方程式等號兩邊相加減之每一項的單位都必須相同。

* 電學單位可利用動能 $\frac{1}{2}mv^2$ 與電能 IVT 、 QV 、 $\frac{1}{2}CV^2$ 、 $\frac{1}{2}LI^2$ 之單位轉換

SI Prefix	G	M	k	m	μ	n	p
10^{3n}	10^9	10^6	10^3	10^{-3}	10^{-6}	10^{-9}	10^{-12}



Example: $R = 22 \times 10^3 \Omega = 22\text{k}\Omega$

$L = 0.3 \times 10^{-3} \text{H} = 0.3\text{mH}$

$C = 4.7 \times 10^{-6} \text{F} = 4.7\mu\text{F}$

1.2 Field Sources and Fields

Field Sources		Electric field		Magnetic field	
		Static	Time-Varying	Static	Time-Varying
Charge	Stationary	■			
	Moving		■		
Current	Direct			■	
	Alternating				■
Electromagnetic wave			■		■

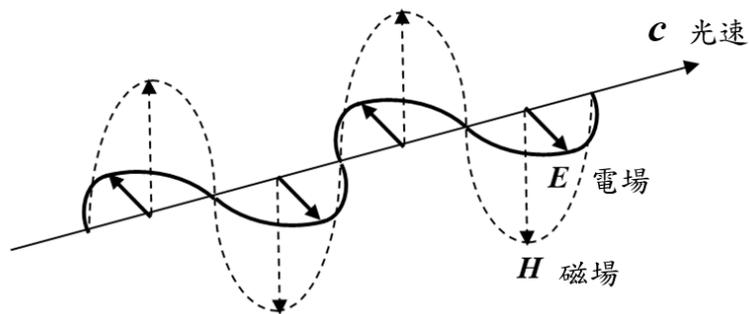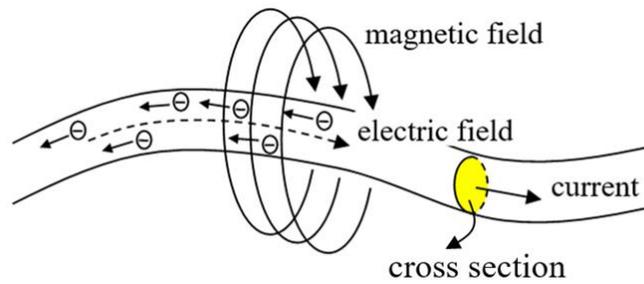

* 質量 m 之電荷 q 受力

重力 $F_m=mg$

電力 $F_E=qE$

磁力 $F_B=qv \times B$

1.3 Electric Charges and Current

- The free charges in an electric wire are electrons, $e^- = -1.602 \times 10^{-19} \text{ C}$.
- The electrons are driven to move by electric field and form a current.
- The current I through the cross section of an electric wire is defined as

$$(1.3-1) \quad I = \frac{\Delta q}{\Delta t} \quad [\text{C/s}]$$

where Δq is the charge through a cross section in a time period Δt .

- Instantaneous current

$$(1.3-2) \quad i(t) = \lim_{\Delta t \rightarrow 0} \frac{\Delta q}{\Delta t} = \frac{q(t+dt) - q(t)}{dt} \Big|_{dt \rightarrow 0} = \frac{dq(t)}{dt}$$

On the other hand,

$$(1.3-3) \quad q(t) = \int_{-\infty}^t i(\tau) d\tau = q(t_0) + \int_{t_0}^t i(\tau) d\tau, \quad q(t_0) = \int_{-\infty}^{t_0} i(\tau) d\tau$$


- Average current in $t \in [t_1, t_2]$

$$(1.3-4) \quad I_{avg} = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} i(\tau) d\tau$$

- * 為何一打開電源開關燈泡瞬間就亮了？是電子在電線中快速移動嗎？
並非如此，主要是因為電源一開就隨即產生電場沿著電線以光速傳遞，此時電線中所有的電子幾乎同時受到電力的作用開始移動，電流彷彿瞬間形成以點亮燈泡，不過真正實景卻是電子移動速度相當緩慢，約 10^{-4} m/s 。
[請嘗試以水龍頭一打開馬上就有自來水流出的情況來解釋。]

Example: (1) If $x(t) = q(t) [\mu\text{C}]$, determine $i(t)$.

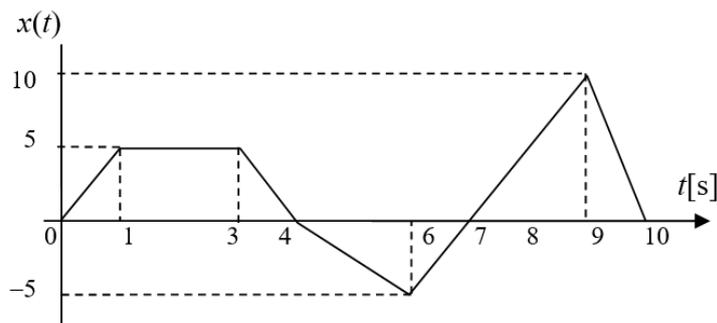(2) If $x(t) = i(t) [\text{mA}]$, determine $q(t)$.



1.4 Voltage and Power

- A charge q moving from P_1 to P_2 consumes electric work

$$(1.4-1) \quad w = q(V_1 - V_2) = qv \quad [\text{J}]$$

where V_1 and V_2 are the potentials at P_1 and P_2 and $v = V_1 - V_2$ is the voltage between P_1 and P_2 .

- Instantaneous power


$$(1.4-2) \quad p(t) = \frac{dw(t)}{dt} = \frac{dw(t)}{dq(t)} \frac{dq(t)}{dt} = v(t)i(t) \quad [\text{W, J/s}]$$

$$\Rightarrow w(t) = w(t_0) + \int_{t_0}^t p(\tau) d\tau$$

- Average power in $t \in [t_1, t_2]$

$$(1.4-3) \quad P_{avg} = \frac{w(t_2) - w(t_1)}{t_2 - t_1} = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} p(\tau) d\tau$$

- Passive Sign Convention (PSC)

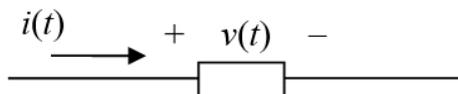


- * 元件上電流 $i(t)$ 的方向與電壓 $v(t)$ 的正負端可以任意選定，但是只有依據 PSC 所選定的 $i(t)$ 與 $v(t)$ ，其乘積 $p(t) = v(t)i(t)$ 才是消耗或儲存在元件上功率。在一般情況下，若未特別標明，元件的電壓與電流視為以 PSC 表示。

Example: Consider a component in an electric circuit. If $v(t) = 3 \sin(\pi t / 3)$ and $i(t) = 4 \cos(\pi t / 3)$, determine the instantaneous power $p(t)$ and the average power P_{avg} for $0 \leq t \leq 1$.

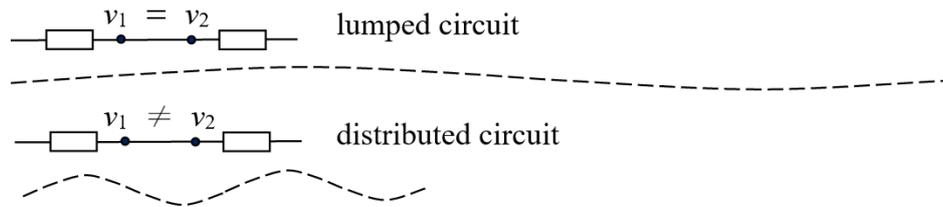1.5 Kirchhoff's Laws

- KVL: Kirchhoff's voltage law
KCL: Kirchhoff's current law
- A lumped circuit is constructed by lumped components with dimension much less than the wavelength of electric waves.



- A loop with n components in series

KVL:
$$\sum_{k=1}^n v_k = 0$$


where v_k is the voltage across the k -th component.

- A node with m components connecting to it

KCL:
$$\sum_{k=1}^m i_k = 0$$

where i_k is the current through the k -th component away(or into) the node.

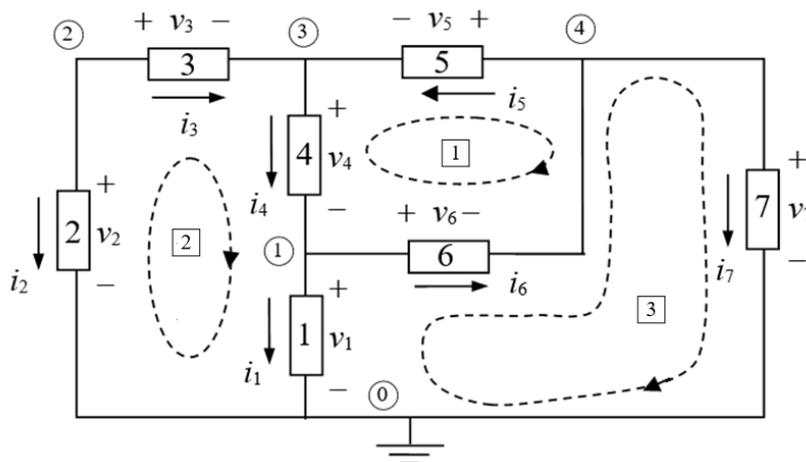Example: Write KVL for the loops ① to ③ and KCL for the nodes ① to ④.



1.6 Conservation of Energy

- The law of conservation of energy

$$(1.6-1) \quad \sum_{k=1}^n w_k(t) = \sum_{k=1}^n \int_{-\infty}^t p_k(\tau) d\tau = \sum_{k=1}^n \int_{-\infty}^t v_k(\tau) i_k(\tau) d\tau = 0$$

which implies


$$(1.6-2) \quad \sum_{k=1}^n w_k(t) = \int_{-\infty}^t \left(\sum_{k=1}^n v_k(\tau) i_k(\tau) \right) d\tau = \int_{-\infty}^t \left(\sum_{k=1}^n p_k(\tau) \right) d\tau = 0.$$

- The total power is also conserved


$$(1.6-3) \quad \sum_{k=1}^n p_k(\tau) = \sum_{k=1}^n v_k(t) i_k(t) = 0$$

1.7 Ideal Sources

- Independent voltage/current sources

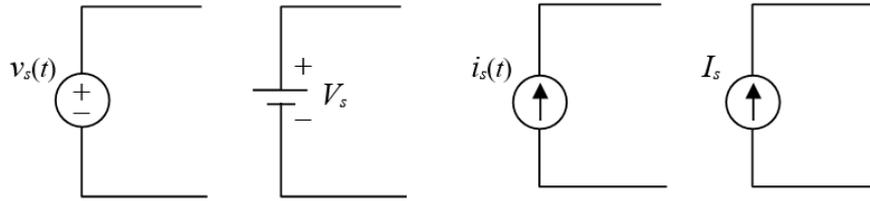

- Dependent Sources

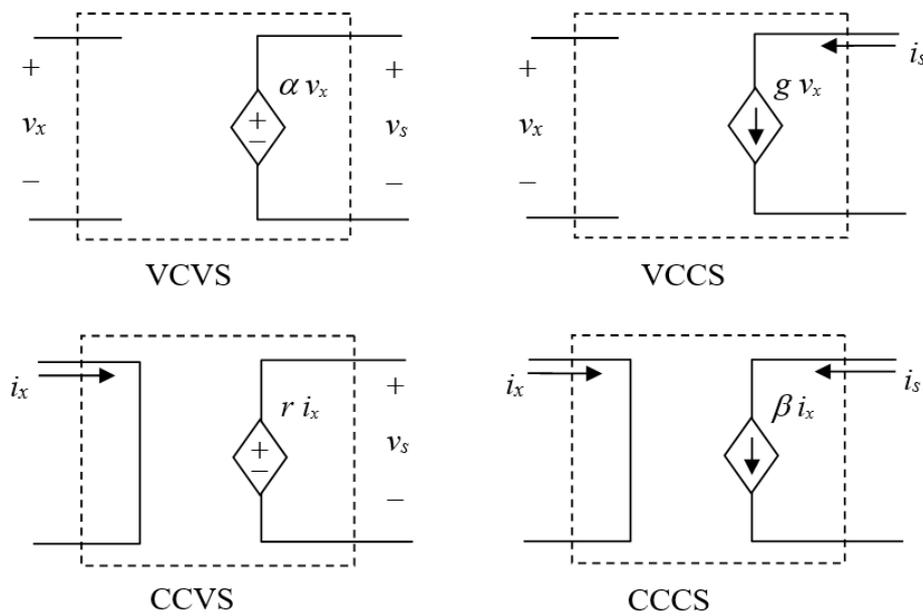


VCVS: Voltage-Controlled Voltage Source

VCCS: Voltage-Controlled Current Source

CCVS: Current-Controlled Voltage Source


CCCS: Current-Controlled Current Source

Example: BJT Transistor, CCCS

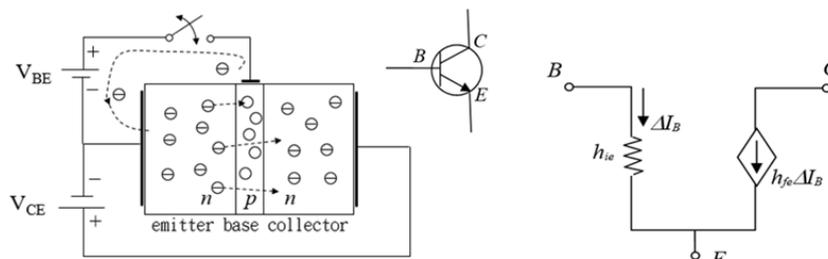


1.8 Resistors

- Nonlinear Resistor

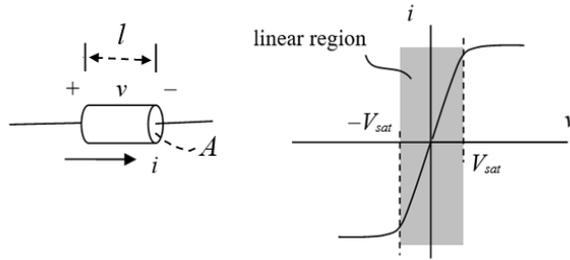

- Linear Resistor

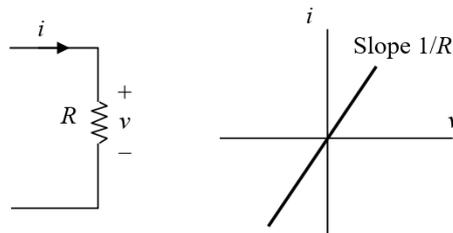

- Resistance

$$(1.8-1) \quad R = \rho \frac{l}{A} \quad [\Omega]$$

ρ : resistivity, A : cross area, l : length

- Ohm's Law

$$(1.8-2) \quad v(t) = R \cdot i(t) \quad \text{or} \quad i(t) = G \cdot v(t)$$


where $G = R^{-1}$ [S] is called the conductance.

- Power dissipated in resistor

$$(1.8-4) \quad p(t) = i(t)v(t) = Ri^2(t) = \frac{v^2(t)}{R} \quad [\text{W}]$$


$$(1.8-5) \quad p(t) = i(t)v(t) = Gv^2(t) = \frac{i^2(t)}{G} \quad [\text{W}]$$

- Open circuit and Short circuit

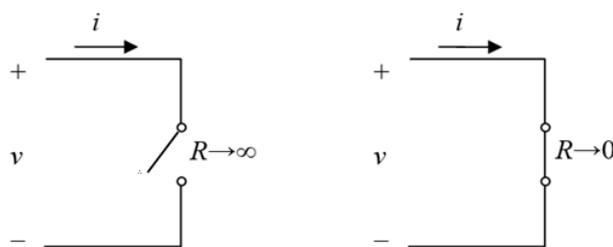

1.9 Resistors in Series and parallel

1.9.1 Resistors in Series

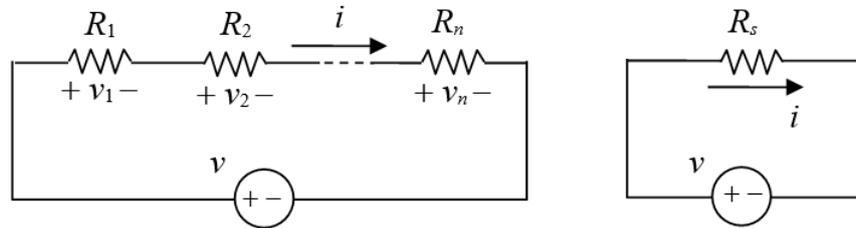

- Mathematic model

$$(1.9.1-1) \quad i_1(t) = i_2(t) = \dots = i_n(t) = i(t)$$

$$(1.9.1-2) \quad v_k(t) = R_k i_k(t) = R_k i(t)$$

$$\text{KVL:} \quad v(t) = v_1(t) + v_2(t) + \dots + v_n(t) = (R_1 + R_2 + \dots + R_n) i(t) = R_s i(t)$$


$$\Rightarrow i(t) = \frac{v(t)}{R_1 + R_2 + \dots + R_n} = \frac{v(t)}{R_s}$$

$$\Rightarrow v_k(t) = R_k i(t) = \frac{R_k}{R_s} v(t)$$

- Equivalent resistance


$$(1.9.1-3) \quad R_s = R_1 + R_2 + \dots + R_n$$

- Practical voltage source

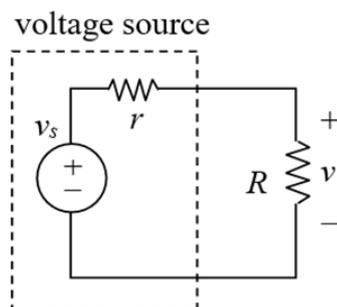

$$(1.9.1-4) \quad v(t) = \frac{R}{R+r} v_s(t), \quad r \ll R$$

1.9.2 Resistors in Parallel

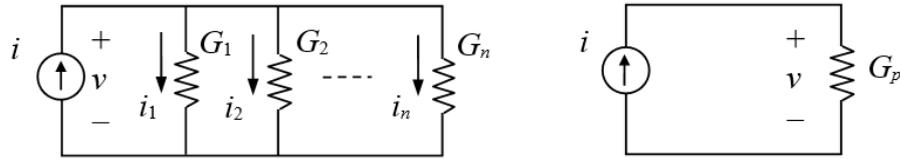

- Mathematic model

$$(1.9.2-1) \quad v_1(t) = v_2(t) = \cdots = v_n(t) = v(t)$$

$$(1.9.2-2) \quad i_k(t) = G_k v_k(t) = G_k v(t)$$

$$\text{KCL:} \quad i(t) = i_1(t) + i_2(t) + \cdots + i_n(t) = (G_1 + G_2 + \cdots + G_n)v(t) = G_p v(t)$$


$$\Rightarrow v(t) = \frac{i(t)}{G_1 + G_2 + \cdots + G_n} = \frac{i(t)}{G_p}$$

$$\Rightarrow i_k(t) = G_k v(t) = \frac{G_k}{G_p} i(t)$$

- Equivalent conductance


$$(1.9.2-3) \quad G_p = G_1 + G_2 + \cdots + G_n \quad \text{or} \quad \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \cdots + \frac{1}{R_n}$$

- Practical current source

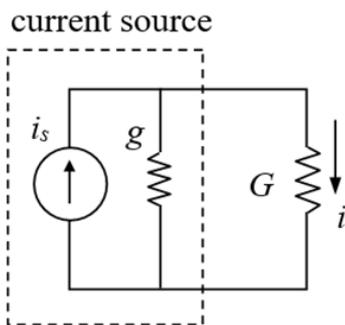


$$(1.9.2-4) \quad i(t) = \frac{G}{G + g} i_s(t), \quad g \ll G$$

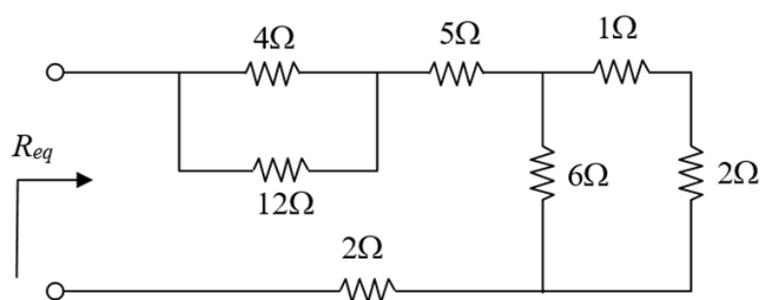Example: Determine the equivalent resistance R_{eq}




Example: Determine the voltage v_0 .

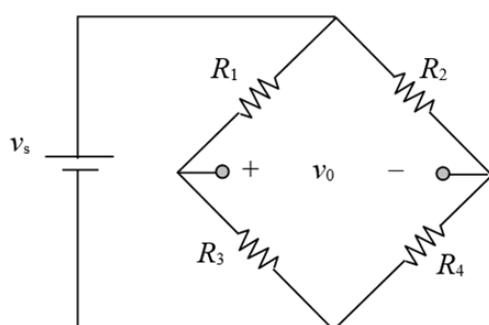

1.10 Capacitors

- Linear capacitor

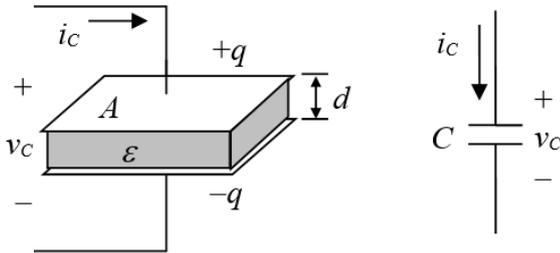

$$(1.10-1) \quad q(t) = Cv_c(t)$$

- Capacitance

$$(1.10-2) \quad C = \varepsilon \frac{A}{d} \quad [\text{F, C/V}]$$

ε : dielectric coefficient, A : plate area, d : distance

- Component equations** (元件方程式)

$$(1.10-3) \quad i_c(t) = C \frac{dv_c(t)}{dt}$$

$$(1.10-4) \quad v_c(t) = \frac{1}{C} \int_{-\infty}^t i_c(\tau) d\tau = v_c(t_0) + \frac{1}{C} \int_{t_0}^t i_c(\tau) d\tau$$

where $v_c(t_0) = \frac{1}{C} \int_{-\infty}^{t_0} i_c(\tau) d\tau$.

- Continuity of capacitor's voltage

$$(1.10-5) \quad v_c(t^-) = v_c(t) = v_c(t^+)$$


- Stored power and energy

$$(1.10-6) \quad p_c(t) = v_c(t)i_c(t) = v_c(t) \left(C \frac{dv_c(t)}{dt} \right) = \frac{d}{dt} \left(\frac{1}{2} Cv_c^2(t) \right)$$

$$(1.10-7) \quad w_c(t) = \int_{t_0}^t p_c(\tau) d\tau = \frac{1}{2} Cv_c^2(\tau) \Big|_{v_c(t_0)}^{v_c(t)} = \frac{1}{2} Cv_c^2(t) - \frac{1}{2} Cv_c^2(t_0)$$

1.11 Capacitors in Series and Parallel

1.11.1 Capacitors in Series

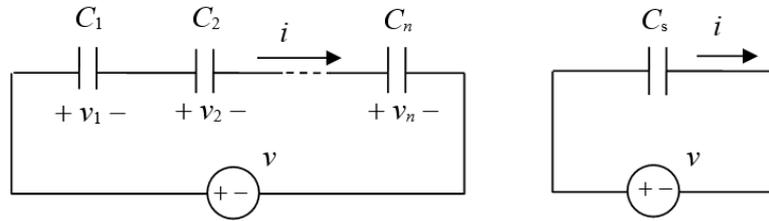

- Mathematic model

$$(1.11.1-1) \quad v(t) = v_1(t) + v_2(t) + \cdots + v_n(t) = \sum_{k=1}^n v_k(t)$$

$$(1.11.1-2) \quad v_k(t) = \frac{1}{C_k} \int_{-\infty}^t i(\tau) d\tau = v_k(t_0) + \frac{1}{C_k} \int_{t_0}^t i(\tau) d\tau$$


$$\begin{aligned} \text{KVL:} \quad v(t) &= \sum_{k=1}^n \frac{1}{C_k} \int_{-\infty}^t i(\tau) d\tau \\ &= \left(\frac{1}{C_1} + \frac{1}{C_2} + \cdots + \frac{1}{C_n} \right) \int_{-\infty}^t i(\tau) d\tau = \frac{1}{C_s} \int_{-\infty}^t i(\tau) d\tau \end{aligned}$$

- Equivalent capacitance

$$(1.11.1-3) \quad \frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \cdots + \frac{1}{C_n}$$

$$(1.11.1-4) \quad C_s = \left(\frac{1}{C_1} + \frac{1}{C_2} + \cdots + \frac{1}{C_n} \right)^{-1}$$

1.11.2 Capacitors in Parallel

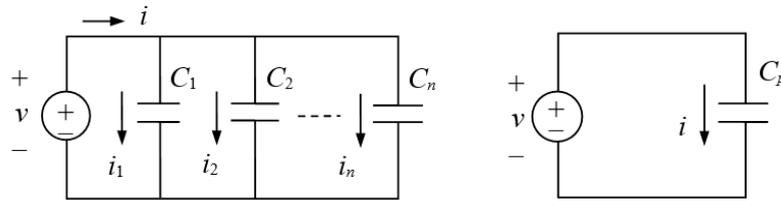

- Mathematic model

$$(1.11.2-1) \quad i(t) = i_1(t) + i_2(t) + \cdots + i_n(t) = \sum_{k=1}^n i_k(t)$$

$$(1.11.2-2) \quad i_k(t) = C_k \frac{dv(t)}{dt}$$

$$\text{KCL:} \quad i(t) = \sum_{k=1}^n C_k \frac{dv(t)}{dt} = (C_1 + C_2 + \cdots + C_n) \frac{dv(t)}{dt} = C_p \frac{dv(t)}{dt}$$


- Equivalent capacitance

$$(1.11-9) \quad C_p = C_1 + C_2 + \cdots + C_n$$


Example: If $C = 4.7 \mu\text{F}$, then

(1) determine $i_c(t)$ for $x(t) = v_c(t)$ [V].

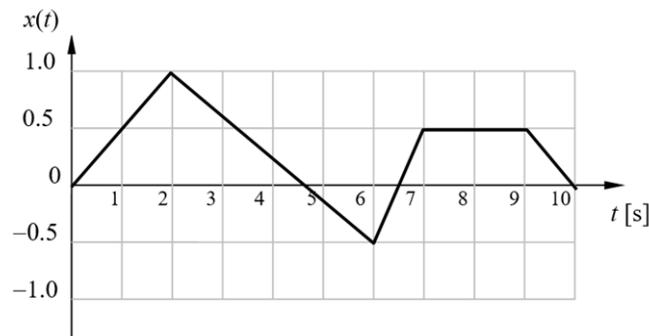(2) determine $v_c(t)$ for $x(t) = i_c(t)$ [A].




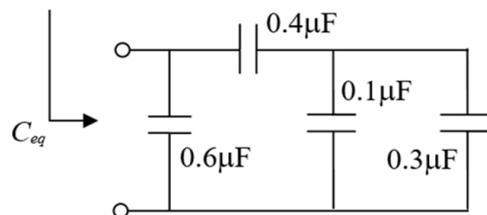Example: Determine the equivalent capacitance C_{eq} .



1.12 Inductors

- Linear inductor

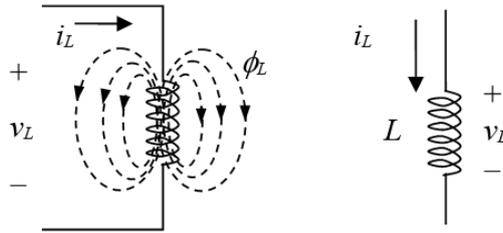

$$(1.12-1) \quad v_L(t) = \frac{d(N\phi_L(t))}{dt}$$

- Inductance

$$(1.12-2) \quad L = \frac{N\phi_L(t)}{i_L(t)} \quad [\text{H}]$$

N : the number of coils.

- Component equation (元件方程式)

$$(1.12-3) \quad v_L(t) = L \frac{di_L(t)}{dt}$$

$$(1.12-4) \quad i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L(\tau) d\tau = i_L(t_0) + \frac{1}{L} \int_{t_0}^t v_L(\tau) d\tau$$

where $i_L(t_0) = \frac{1}{L} \int_{-\infty}^{t_0} v_L(\tau) d\tau$.

- Continuity of inductor's current

$$(1.12-5) \quad i_L(t^-) = i_L(t) = i_L(t^+)$$


- Stored power and energy

$$(1.12-6) \quad p_L(t) = v_L(t)i_L(t) = \left(L \frac{di_L(t)}{dt} \right) i_L(t) = \frac{d}{dt} \left(\frac{1}{2} Li_L^2(t) \right)$$

$$(1.12-7) \quad w_L(t) = \int_{t_0}^t p_L(\tau) d\tau = \frac{1}{2} Li_L^2(\tau) \Big|_{i_L(t_0)}^{i_L(t)} = \frac{1}{2} Li_L^2(t) - \frac{1}{2} Li_L^2(t_0)$$

1.13 Inductors in Series and Parallel

1.13.1 Inductors in Series

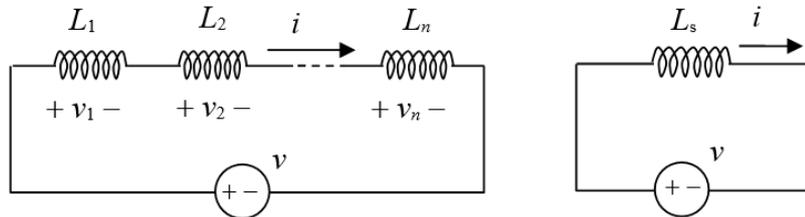

- Mathematic model

$$(1.13.1-1) \quad v(t) = v_1(t) + v_2(t) + \cdots + v_n(t) = \sum_{k=1}^n v_k(t)$$


$$(1.13.1-2) \quad v_k(t) = L_k \frac{di(t)}{dt}$$

$$\text{KVL:} \quad v(t) = \sum_{k=1}^n L_k \frac{di(t)}{dt} = (L_1 + L_2 + \cdots + L_n) \frac{di(t)}{dt} = L_s \frac{di(t)}{dt}$$

- Equivalent inductance

$$(1.13-4) \quad L_s = L_1 + L_2 + \cdots + L_n$$

1.13.2 Inductors in Parallel

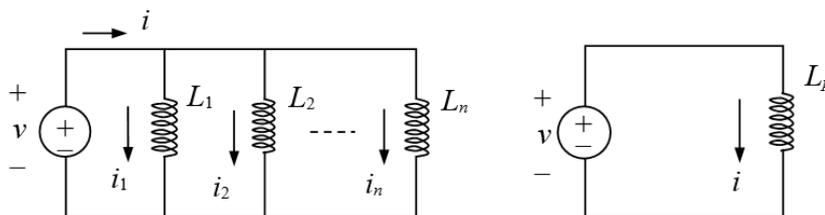

- Mathematic model

$$(1.13.1-1) \quad i(t) = i_1(t) + i_2(t) + \cdots + i_n(t) = \sum_{k=1}^n i_k(t)$$

$$(1.13.2-2) \quad i_k(t) = \frac{1}{L_k} \int_{-\infty}^t v(\tau) d\tau = i_k(t_0) + \frac{1}{L_k} \int_{t_0}^t v(\tau) d\tau$$

$$\begin{aligned} \text{KCL: } i(t) &= \sum_{k=1}^n \frac{1}{L_k} \int_{-\infty}^t v(\tau) d\tau \\ &= \left(\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n} \right) \int_{-\infty}^t v(\tau) d\tau = \frac{1}{L_p} \int_{-\infty}^t v(\tau) d\tau \end{aligned}$$


- Equivalent inductance

$$(1.13-8) \quad \frac{1}{L_p} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$$

$$(1.13-9) \quad L_p = \left(\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n} \right)^{-1}$$

Example: If $L = 0.3 \text{ mH}$, then

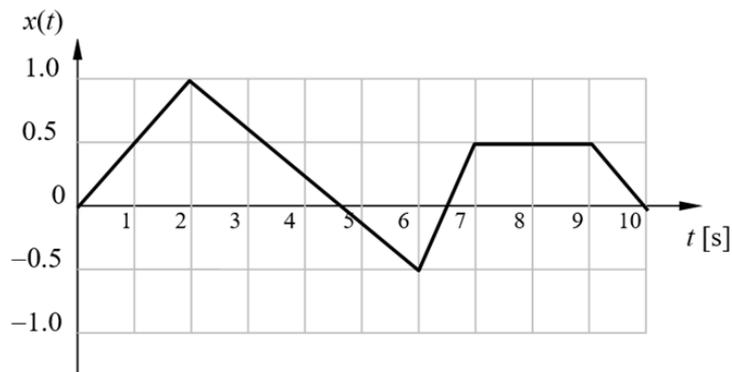- (1) determine $i_L(t)$ for $x(t) = v_L(t)$ [V].
- (2) determine $v_L(t)$ for $x(t) = i_L(t)$ [A].



Example: Determine the equivalent inductance L_{eq} .

