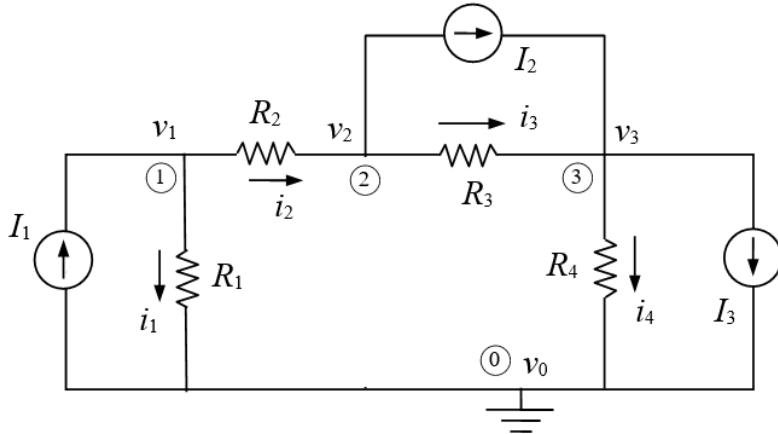


## Chap 2 Resistive Circuits

### 2.1 Node-Voltage Analysis

#### 2.1.1 Independent current sources

- Resistive circuit with only independent current sources  $I_1$ ,  $I_2$  and  $I_3$



Reference node: ④, Reference voltage:  $v_0 = 0$

Nodes: ①, ②, ③, Node voltages referring to  $v_0$ :  $v_1$ ,  $v_2$ ,  $v_3$

Unknown voltages to be solved:  $v_1$ ,  $v_2$ ,  $v_3$

- Node voltage equations

$$\text{KCL}①: i_1 + i_2 - I_1 = \frac{v_1}{R_1} + \frac{v_1 - v_2}{R_2} - I_1 = 0$$

$$\text{KCL}②: -i_2 + i_3 + I_2 = \frac{v_2 - v_1}{R_2} + \frac{v_2 - v_3}{R_3} + I_2 = 0$$

$$\text{KCL}③: -i_3 + i_4 - I_2 + I_3 = \frac{v_3 - v_2}{R_3} + \frac{v_3}{R_4} - I_2 + I_3 = 0$$

- In terms of conductances,

$$\text{KCL}①: (G_1 + G_2)v_1 - G_2 v_2 = I_1$$

$$\text{KCL}②: -G_2 v_1 + (G_2 + G_3)v_2 - G_3 v_3 = -I_2$$

$$\text{KCL}③: -G_3 v_2 + (G_3 + G_4)v_3 = I_2 - I_3$$

- In matrix form,

$$(2.1.1-1) \quad \underbrace{\begin{bmatrix} G_1+G_2 & -G_2 & 0 \\ -G_2 & G_2+G_3 & -G_3 \\ 0 & -G_3 & G_3+G_4 \end{bmatrix}}_A \cdot \underbrace{\begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}}_{\boldsymbol{v}} = \underbrace{\begin{bmatrix} 1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & 1 & -1 \end{bmatrix}}_B \cdot \underbrace{\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}}_{\boldsymbol{u}}$$


$$\Rightarrow \boldsymbol{v} = [v_1 \ v_2 \ v_3]^T = \mathbf{A}^{-1} \mathbf{B} \boldsymbol{u}$$

- $\mathbf{A}$  : symmetric positive-definite,  $\mathbf{A}^{-1}$  exists
- All the component's voltages and currents can be obtained in terms of the node

voltages. For example,  $i_1 = \frac{v_1}{R_1}$ ,  $i_2 = \frac{v_1 - v_2}{R_2}$ ,  $i_3 = \frac{v_2 - v_3}{R_3}$ ,  $i_4 = \frac{v_3}{R_4}$ .
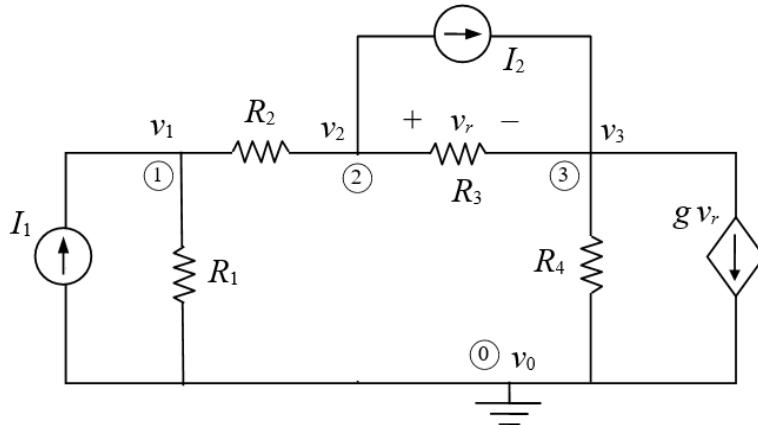
## 2.1.2 Dependent current sources

- Resistive circuit with only current sources including at least one dependent current source such as  $g v_r$ , where  $v_r = v_2 - v_3$ .



- Node voltage equations

$$\text{KCL}①: \quad \frac{v_1}{R_1} + \frac{v_1 - v_2}{R_2} - I_1 = 0$$

$$\text{KCL}②: \quad \frac{v_2 - v_1}{R_2} + \frac{v_2 - v_3}{R_3} + I_2 = 0$$

$$\text{KCL}③: \quad -i_3 + i_4 - I_2 + g v_r = \frac{v_3 - v_2}{R_3} + \frac{v_3}{R_4} - I_2 + g(v_2 - v_3) = 0$$

- In terms of conductances,

$$\text{KCL}①: (G_1 + G_2)v_1 - G_2 v_2 = I_1$$

$$\text{KCL}②: -G_2 v_1 + (G_2 + G_3)v_2 - G_3 v_3 = -I_2$$

$$\text{KCL}③: (-G_3 + g)v_2 + (G_3 + G_4 - g)v_3 = I_2$$


- In matrix form,

$$(2.1.2-1) \quad \underbrace{\begin{bmatrix} G_1+G_2 & -G_2 & 0 \\ -G_2 & G_2+G_3 & -G_3 \\ 0 & -G_3+g & G_3+G_4-g \end{bmatrix}}_A \cdot \underbrace{\begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}}_v = \underbrace{\begin{bmatrix} 1 & 0 \\ 0 & -1 \\ 0 & 1 \end{bmatrix}}_B \cdot \underbrace{\begin{bmatrix} I_1 \\ I_2 \\ u \end{bmatrix}}_u$$

- If  $g \neq G_3 + G_4 + G_3G_4 \frac{G_1+G_2}{G_1G_2}$ , then  $A$  is invertible and  $v = A^{-1}Bu$ .
- All the component's voltages and currents in the resistive circuit can be expressed in terms of the node voltages.
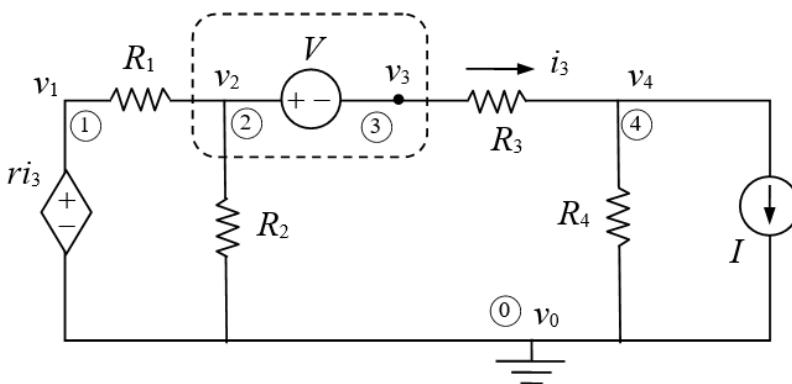
### 2.1.3 Voltage sources

- Resistive circuit including at least one voltage source such as independent voltage source  $V$  and dependent voltage source  $ri_3$ , where  $i_3 = \frac{v_3 - v_4}{R_3}$ .
- Supernode'②③'.



- Node voltage equations

$$\text{KVL}①: v_1 = ri_3 = r \left( \frac{v_3 - v_4}{R_3} \right)$$

$$\text{KCL(2)(3)} : \frac{v_2 - v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3 - v_4}{R_3} = 0$$

$$\text{KVL(2)(3)} : v_2 - v_3 = V$$

$$\text{KCL(4)} : \frac{v_4 - v_3}{R_3} + \frac{v_4}{R_4} + I = 0$$

- In terms of conductances,

$$\text{KVL(1)} : v_1 - rG_3v_3 + rG_3v_4 = 0$$

$$\text{KCL(2)(3)} : -G_1v_1 + (G_1 + G_2)v_2 + G_3v_3 - G_3v_4 = 0$$

$$\text{KVL(2)(3)} : v_2 - v_3 = V$$


$$\text{KCL(4)} : -G_3v_3 + (G_3 + G_4)v_4 = -I$$

- In matrix form,

$$(2.1.3-1) \quad \underbrace{\begin{bmatrix} 1 & 0 & -rG_3 & rG_3 \\ -G_1 & G_1 + G_2 & G_3 & -G_3 \\ 0 & 1 & -1 & 0 \\ 0 & 0 & -G_3 & G_3 + G_4 \end{bmatrix}}_A \cdot \underbrace{\begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix}}_v = \underbrace{\begin{bmatrix} 0 & 0 \\ 0 & 0 \\ 1 & 0 \\ 0 & -1 \end{bmatrix}}_B \cdot \underbrace{\begin{bmatrix} V \\ I \end{bmatrix}}_u$$

- If  $r \neq \frac{1}{G_1} + \left( \frac{1}{G_3} + \frac{1}{G_4} \right) \left( 1 + \frac{G_2}{G_1} \right)$ , then  $A$  is invertible and  $v = A^{-1}Bu$ .
- All the component's voltages and currents in the resistive circuit can be expressed in terms of the node voltages.

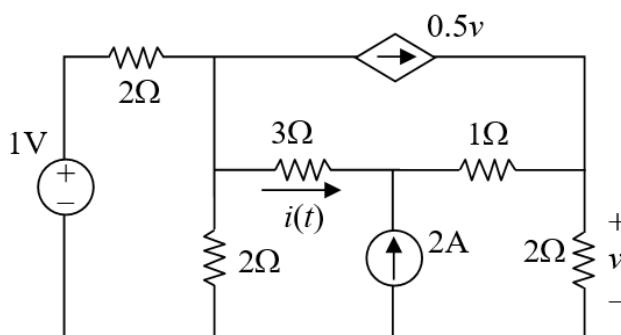Example: Based on node voltage analysis, determine  $i(t)$ .




## 2.2 Mesh-Current Analysis

- Unlike the node-voltage analysis, the mesh-current analysis is only suitable for planar circuit.
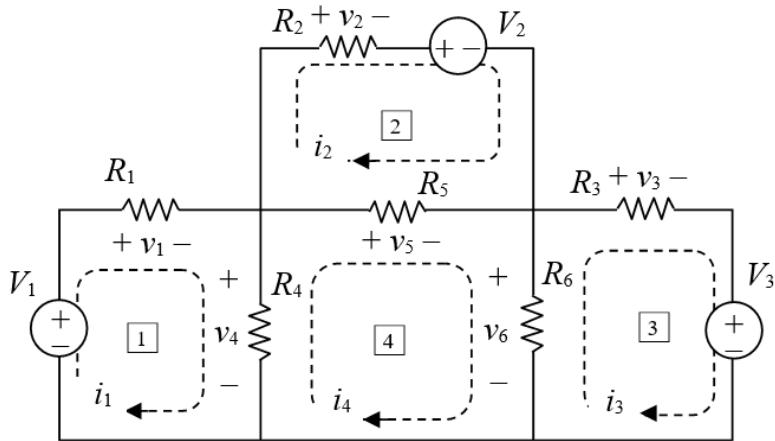
### 2.2.1 Independent voltage sources

- Resistive circuit with only independent voltage sources  $V_1$ ,  $V_2$  and  $V_3$



Meshes:  $\boxed{1}$ ,  $\boxed{2}$ ,  $\boxed{3}$ ,  $\boxed{4}$ , Mesh currents:  $i_1$ ,  $i_2$ ,  $i_3$ ,  $i_4$

Unknown currents to be solved:  $i_1$ ,  $i_2$ ,  $i_3$ ,  $i_4$

- Mesh current equations

$$\text{KVL} \boxed{1}: \quad v_1 + v_4 - V_1 = R_1 i_1 + R_4 (i_1 - i_4) - V_1 = 0$$

$$\text{KVL} \boxed{2}: \quad v_2 + V_2 - v_5 = R_2 i_2 + V_2 - R_5 (i_4 - i_2) = 0$$

$$\text{KVL} \boxed{3}: \quad v_3 + V_3 - v_6 = R_3 i_3 + V_3 - R_6 (i_4 - i_3) = 0$$

$$\text{KVL} \boxed{4}: \quad v_5 + v_6 - v_4 = R_5 (i_4 - i_2) + R_6 (i_4 - i_3) - R_4 (i_1 - i_4) = 0$$

- In terms of resistance,

$$\text{KVL} \boxed{1}: \quad (R_1 + R_4) i_1 - R_4 i_4 = V_1$$

$$\text{KVL} \boxed{2}: \quad (R_2 + R_5) i_2 - R_5 i_4 = -V_2$$

$$\text{KVL} \boxed{3}: \quad (R_3 + R_6) i_3 - R_6 i_4 = -V_3$$

$$\text{KVL} \boxed{4}: \quad -R_4 i_1 - R_5 i_2 - R_6 i_3 + (R_4 + R_5 + R_6) i_4 = 0$$

- In matrix form,


$$(2.2.1-1) \quad \begin{bmatrix} R_1 + R_4 & 0 & 0 & -R_4 \\ 0 & R_2 + R_5 & 0 & -R_5 \\ 0 & 0 & R_3 + R_6 & -R_6 \\ -R_4 & -R_5 & -R_6 & R_4 + R_5 + R_6 \end{bmatrix} \cdot \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & 0 & -1 \\ 0 & 0 & 0 \end{bmatrix} \cdot \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ \mathbf{u} \end{bmatrix}$$

$$\Rightarrow \mathbf{i} = [i_1 \ i_2 \ i_3 \ i_4]^T = \mathbf{A}^{-1} \mathbf{B} \mathbf{u}$$

- $\mathbf{A}$  is symmetric positive-definite,  $\mathbf{A}^{-1}$  exists.
- All the component's voltages and currents can be obtained in terms of the mesh currents. For example,  $v_1 = R_1 i_1$ ,  $v_3 = R_3 i_3$ ,  $v_5 = R_5 (i_4 - i_2)$ ,  $v_6 = R_6 (i_4 - i_3)$ .
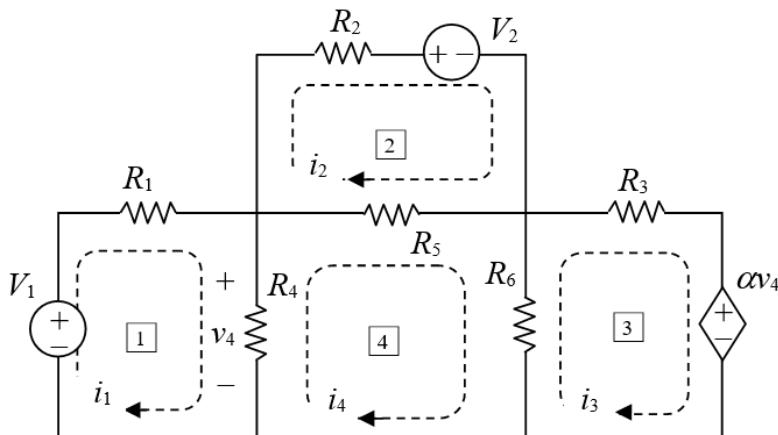
## 2.2.2 Dependent voltage sources

- Resistive circuit with only voltage sources including at least one dependent voltage source, such as  $\alpha v_4$ , where  $v_4 = R_4 (i_1 - i_4)$ .



- Based on KVL, mesh current equations are expressed as

$$\text{KVL}_{\boxed{1}}: R_1 i_1 + R_4 (i_1 - i_4) - V_1 = 0$$

$$\text{KVL}_{\boxed{2}}: R_2 i_2 + V_2 + R_5 (i_2 - i_4) = 0$$

$$\text{KVL}_{\boxed{3}}: R_3 i_3 + \alpha v_4 + R_6 (i_3 - i_4) = R_3 i_3 + \alpha R_4 (i_1 - i_4) + R_6 (i_3 - i_4) = 0$$

$$\text{KVL}_{\boxed{4}}: R_5 (i_4 - i_2) + R_6 (i_4 - i_3) + R_4 (i_4 - i_1) = 0$$

- In terms of resistance,

$$\text{KVL[1]}: (R_1 + R_4)i_1 - R_4 i_4 = V_1$$

$$\text{KVL[2]}: (R_2 + R_5)i_2 - R_5 i_4 = -V_2$$

$$\text{KVL[3]}: \alpha R_4 i_1 + (R_3 + R_6)i_3 - (\alpha R_4 + R_6)i_4 = 0$$

$$\text{KVL[4]}: -R_4 i_1 - R_5 i_2 - R_6 i_3 + (R_4 + R_5 + R_6)i_4 = 0$$

- In matrix form,

$$(2.2.2-1) \quad \underbrace{\begin{bmatrix} R_1 + R_4 & 0 & 0 & -R_4 \\ 0 & R_2 + R_5 & 0 & -R_5 \\ \alpha R_4 & 0 & R_3 + R_6 & -\alpha R_4 - R_6 \\ -R_4 & -R_5 & -R_6 & R_4 + R_5 + R_6 \end{bmatrix}}_A \cdot \underbrace{\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix}}_i = \underbrace{\begin{bmatrix} 1 & 0 \\ 0 & -1 \\ 0 & 0 \\ 0 & 0 \end{bmatrix}}_B \cdot \underbrace{\begin{bmatrix} V_1 \\ V_2 \\ \\ \end{bmatrix}}_u$$


- If  $\alpha \neq 1 + \frac{R_3}{R_6} + R_3 \left( \frac{1}{R_1} + \frac{1}{R_4} \right) + \frac{R_2 R_5}{R_2 + R_5} \left( 1 + \frac{R_3}{R_6} \right) \left( \frac{1}{R_1} + \frac{1}{R_4} \right)$ , then  $A^{-1}$  exists and

$$(2.2.2-2) \quad i = A^{-1}Bu$$

- All the component's voltages and currents in the resistive circuit can be obtained in terms of the mesh currents.
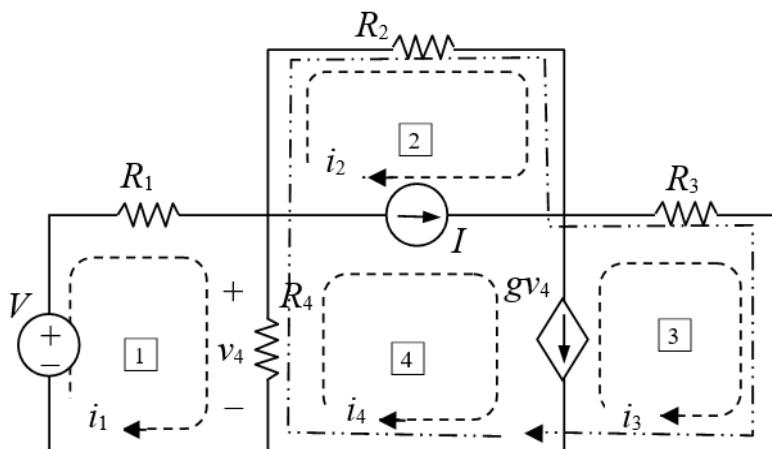
### 2.2.3 Current sources

- Resistive circuit including at least one current source such as independent current source  $I$  and dependent current source  $gv_4$ , where  $v_4 = R_4(i_1 - i_4)$ .



- Supermesh '[2][3][4]'.

- Mesh current equations

$$\text{KVL}[1]: \quad R_1 i_1 + R_4 (i_1 - i_4) - V = 0$$

$$\text{KVL}[2][3][4] : \quad R_2 i_2 + R_3 i_3 + R_4 (i_4 - i_1) = 0$$

$$\text{KCL}[2][3][4] : \quad i_3 - i_4 = -g v_4 = -g R_4 (i_1 - i_4)$$

$$\text{KCL}[2][3][4] : \quad i_4 - i_2 = I$$

- In terms of resistance,

$$\text{KVL}[1]: \quad (R_1 + R_4) i_1 - R_4 i_4 = V$$

$$\text{KVL}[2][3][4] : \quad -R_4 i_1 + R_2 i_2 + R_3 i_3 + R_4 i_4 = 0$$

$$\text{KCL}[2][3][4] : \quad g R_4 i_1 + i_3 - (1 + g R_4) i_4 = 0$$

$$\text{KCL}[2][3][4] : \quad -i_2 + i_4 = I$$


- In matrix form,

$$(2.2.3-1) \quad \underbrace{\begin{bmatrix} R_1 + R_4 & 0 & 0 & -R_4 \\ -R_4 & R_2 & R_3 & R_4 \\ g R_4 & 0 & 1 & -1 - g R_4 \\ 0 & -1 & 0 & 1 \end{bmatrix}}_A \cdot \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 0 \\ 0 & 0 \\ 0 & 1 \end{bmatrix} \cdot \begin{bmatrix} V \\ I \\ u \end{bmatrix}$$

Since  $g \neq -\left(\frac{1}{R_1} + \frac{1}{R_4}\right)\left(1 + \frac{R_2}{R_3}\right) - \frac{1}{R_3}$ ,  $A$  is invertible and  $\mathbf{i} = \mathbf{A}^{-1} \mathbf{B} \mathbf{u}$ .


- All the component's voltages and currents in the resistive circuit can be expressed in terms of the mesh currents.

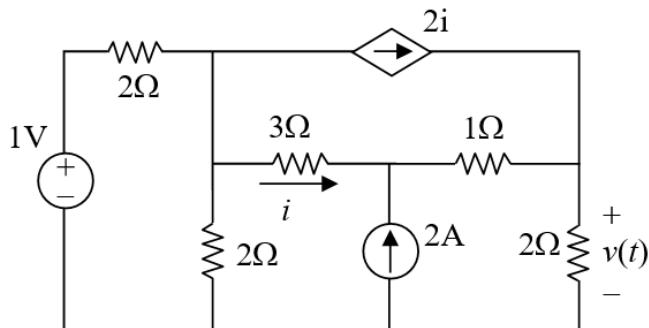Example: Based on mesh current analysis, determine  $v(t)$ .



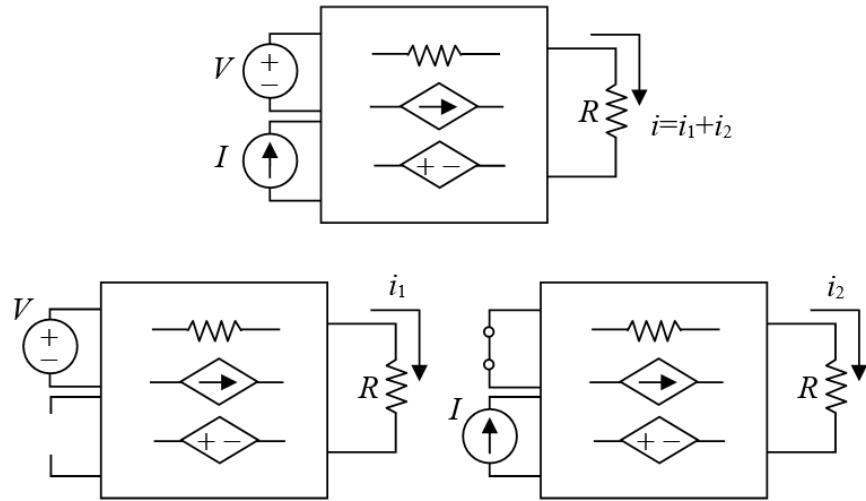
## 2.3 Principle of Superposition

- Resistive circuit with independent voltage source  $V$  and current source  $I$





Example: Determine  $v_o$ .

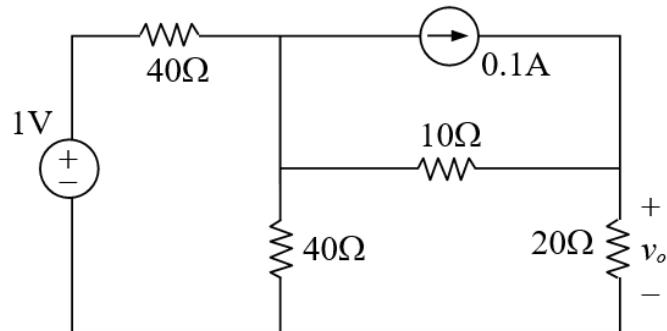

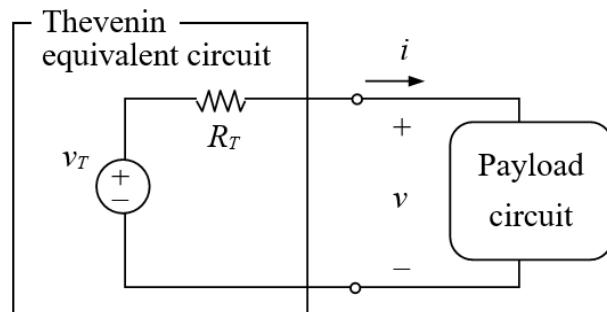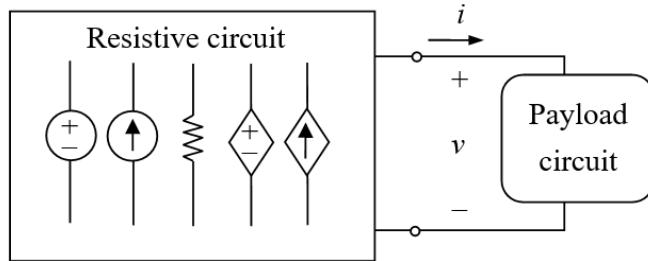
## 2.4 Thevenin Equivalent Circuits

- Resistive circuit with Independent sources




$$(2.4-1) \quad v_T = v + R_T i$$

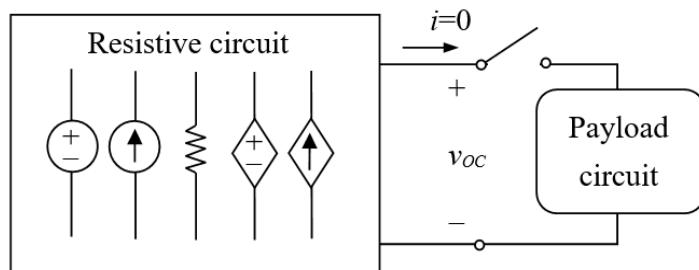- Thevenin equivalent voltage  $v_T = v_{oc}$




- Thevenin equivalent resistance  $R_T$

[A] Without dependent sources



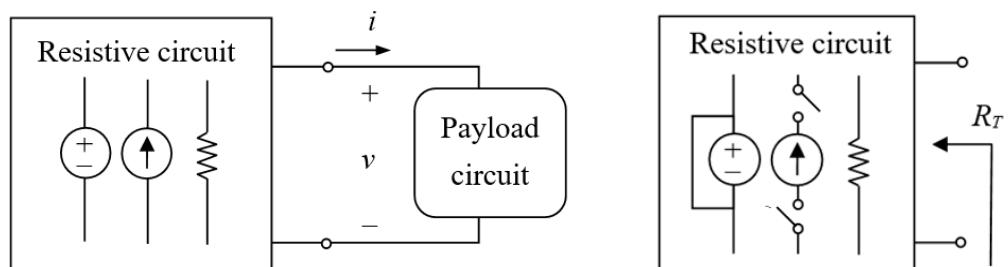


## [B] With dependent sources

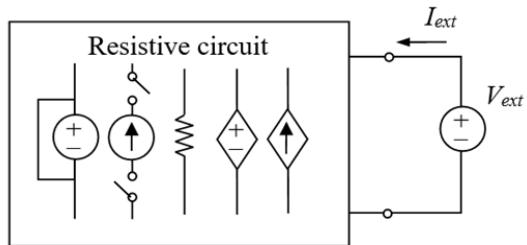



$$(2.4-2) \quad R_T = \frac{V_{ext}}{I_{ext}}$$

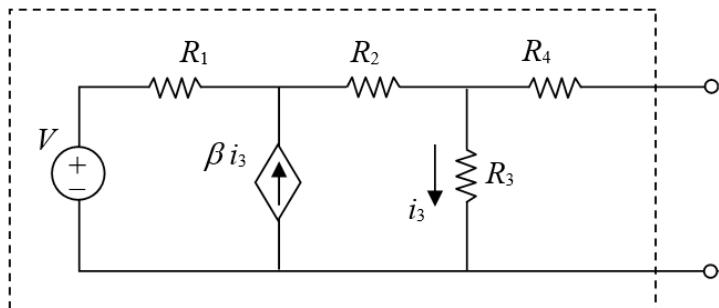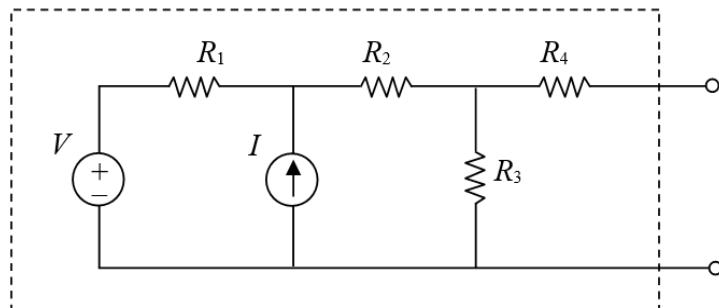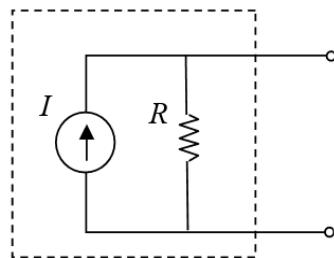Example: Determine the Thevenin equivalent circuit.



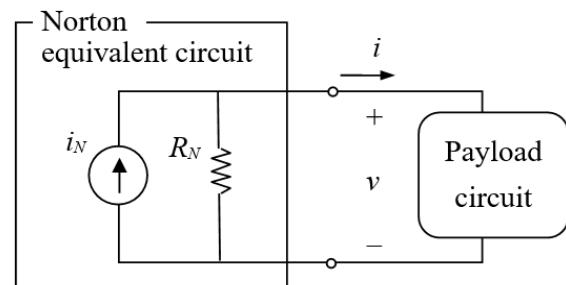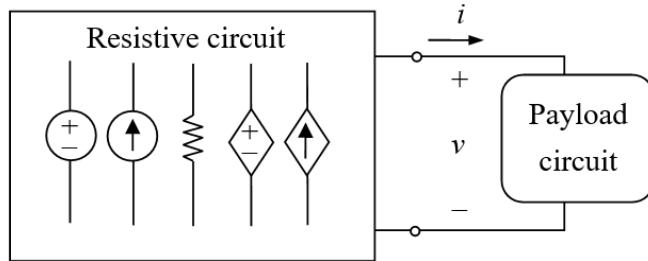
## 2.5 Norton Equivalent Circuits

- Resistive circuit with independent sources




$$(2.5-1) \quad i_N = i + \frac{v}{R_N}$$

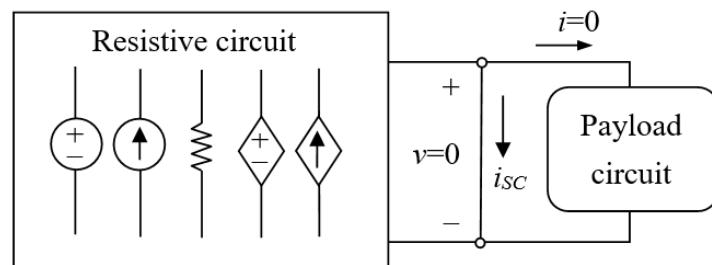- Norton equivalent current  $i_N = i_{SC}$




- Norton equivalent resistance  $R_N$

[A] Without dependent sources



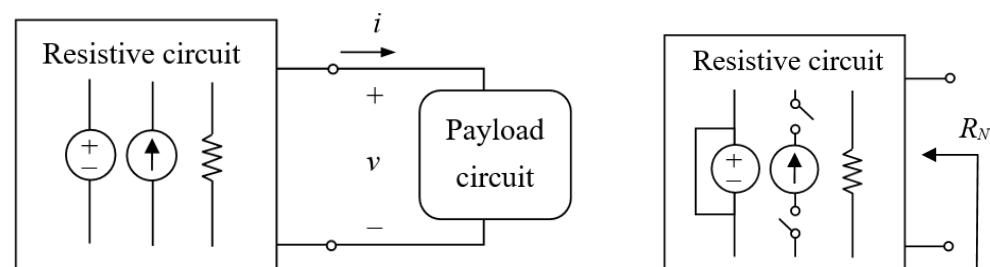


## [B] With dependent sources

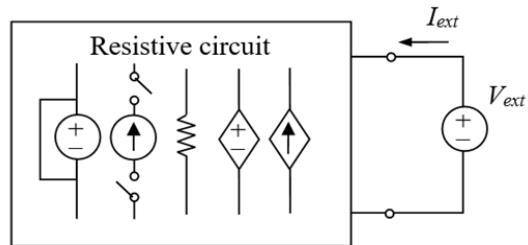


$$(2.5-2) \quad R_N = \frac{V_{ext}}{I_{ext}}$$

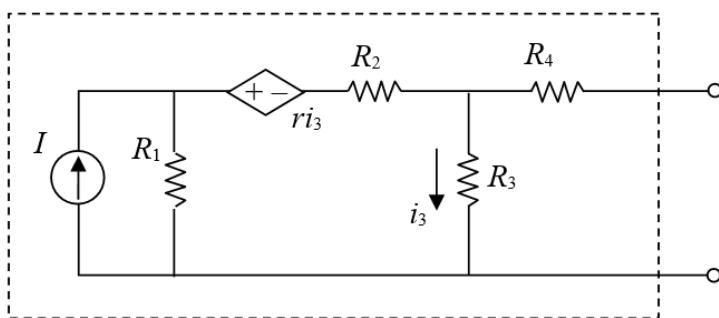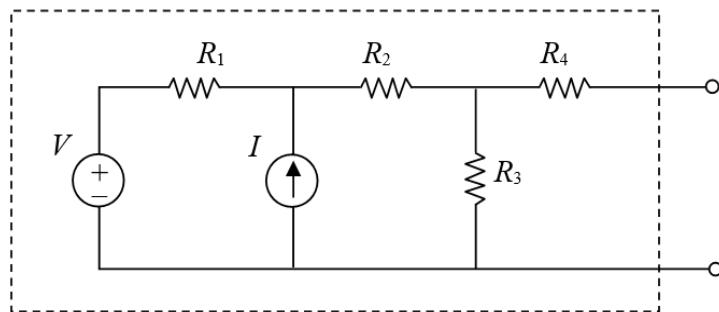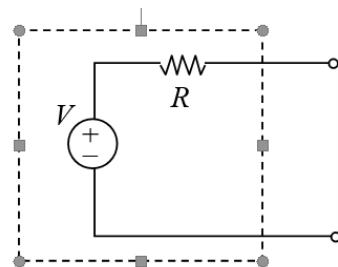Example: Determine the Norton equivalent circuit.


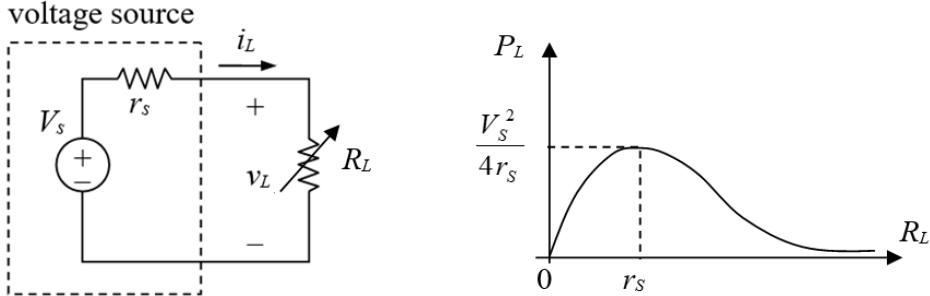
## 2.6 Maximum Power Transfer Theorem

- The power transferred from voltage source to adjustable  $R_L$



$$(2.6-1) \quad i_L = \frac{V_s}{r_s + R_L}, \quad v_L = R_L i_L = \frac{R_L V_s(t)}{r_s + R_L}$$

The power provided by voltage source

$$(2.6-2) \quad P_S = V_s i_L = \frac{V_s^2}{r_s + R_L}$$

The power transferred to  $R_L$

$$(2.6-3) \quad P_L = i_L v_L = \frac{R_L V_s^2(t)}{(r_s + R_L)^2} = \frac{R_L}{r_s + R_L} P_S$$


The derivatives of  $P_L$  with respect to  $R_L$  are

$$\frac{dP_L}{dR_L} = \frac{(r_s - R_L)V_s^2(t)}{(r_s + R_L)^3} \quad \text{and} \quad \frac{d^2P_L}{dR_L^2} = \frac{-2(2r_s - R_L)V_s^2(t)}{(r_s + R_L)^4}$$


Since  $\left. \frac{dP_L}{dR_L} \right|_{R_L=r_s} = 0$  and  $\left. \frac{d^2P_L}{dR_L^2} \right|_{R_L=r_s} < 0$ , the maximum transferred power is

$$(2.6-4) \quad P_{L,max} = P_L \Big|_{R_L=r_s} = \frac{V_s^2(t)}{4r_s} = \frac{1}{2} P_S \Big|_{R_L=r_s}$$

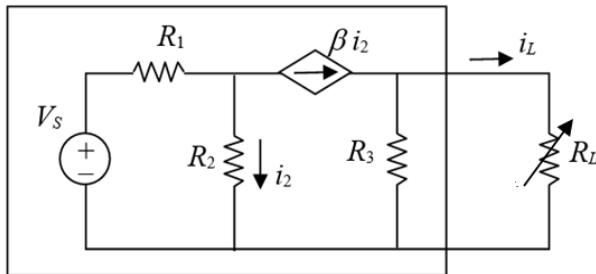
Example: Determine the maximum transferred power to adjustable  $R_L$ .


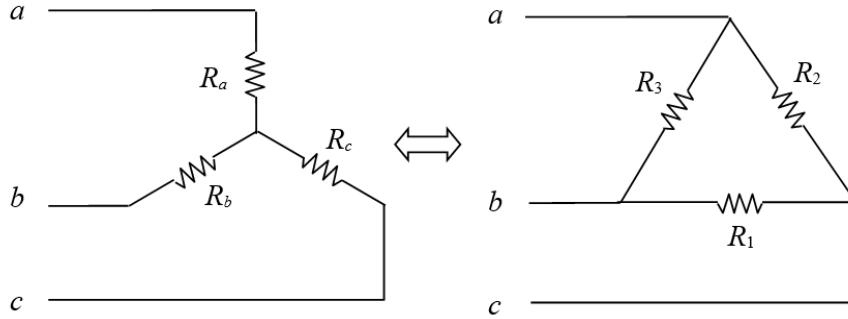
## 2.7 Y-Δ Resistive Circuit Transformation



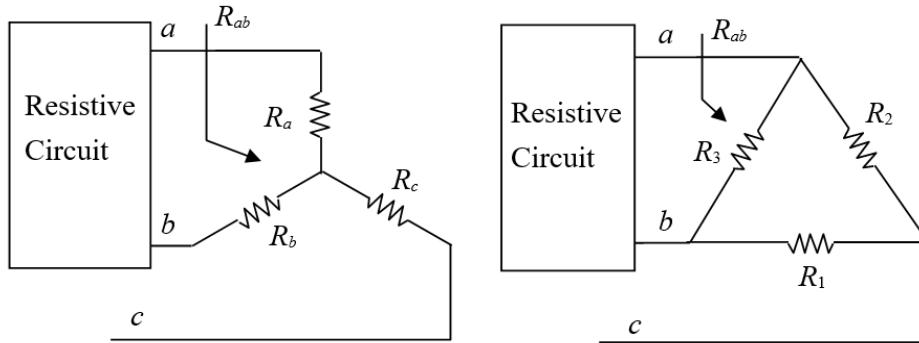- Resistance  $R_{ab}$  with terminal  $c$  open



$$(2.7-1) \quad R_a + R_b = R_3 \parallel (R_1 + R_2) = \frac{R_3(R_1 + R_2)}{R_1 + R_2 + R_3} = \frac{R_2 R_3 + R_3 R_1}{R_1 + R_2 + R_3}$$

- The relation between Y-type and Δ-type resistive circuits

$$(2.7-2) \quad \left\{ \begin{array}{l} R_a + R_b = \frac{R_3(R_1 + R_2)}{R_1 + R_2 + R_3} \\ R_b + R_c = \frac{R_1(R_2 + R_3)}{R_1 + R_2 + R_3} \\ R_c + R_a = \frac{R_2(R_3 + R_1)}{R_1 + R_2 + R_3} \end{array} \right. \Rightarrow R_a + R_b + R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1 + R_2 + R_3}$$

Hence,

$$(2.7-3) \quad R_a = \frac{R_2 R_3}{R_1 + R_2 + R_3}, \quad R_b = \frac{R_3 R_1}{R_1 + R_2 + R_3}, \quad R_c = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

which results in

$$(2.7-4) \quad R_1 R_a = R_2 R_b = R_3 R_c = \frac{R_1 R_2 R_3}{R_1 + R_2 + R_3}$$

$$(2.7-5) \quad \left\{ \begin{array}{l} R_a R_b = \frac{R_3 (R_1 R_2 R_3)}{(R_1 + R_2 + R_3)^2} \\ R_b R_c = \frac{R_1 (R_1 R_2 R_3)}{(R_1 + R_2 + R_3)^2} \\ R_c R_a = \frac{R_2 (R_1 R_2 R_3)}{(R_1 + R_2 + R_3)^2} \end{array} \right. \Rightarrow R_a R_b + R_b R_c + R_c R_a = \frac{R_1 R_2 R_3}{R_1 + R_2 + R_3}$$

From (2.7-4) and (2.7-5), we have

$$(2.7-6) \quad R_1 R_a = R_2 R_b = R_3 R_c = R_a R_b + R_b R_c + R_c R_a$$

which leads to

$$(2.7-7) \quad R_1 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a}$$

$$(2.7-8) \quad R_2 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b}$$

$$(2.7-9) \quad R_3 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c}$$

$$\underbrace{\frac{R_1 R_2 R_3}{R_1 + R_2 + R_3}}_{\text{from } \Delta \text{ to Y}} = R_1 R_a = R_2 R_b = R_3 R_c = R_a R_b + R_b R_c + R_c R_a$$

from Y to  $\Delta$

Example: Determine  $v(t)$ .

