

Chap 5 Phasor Method

5.1 Fundamental concept of phasor method

- Consider an 3rd-order RLC circuit excited by $v(t) = V \cos(\omega t)$

$$(5.1-1) \quad y'''(t) + a_2 y''(t) + a_1 y'(t) + a_0 y(t) = b_2 v''(t) + b_1 v'(t) + b_0 v(t)$$

where $y(t)$ is the voltage or current of a component to be measured.

- The characteristic equation is $\lambda^3 + a_2 \lambda^2 + a_1 \lambda + a_0 = 0$ with roots $Re(\lambda_i) < 0$, $i=1,2,3$, which implies the circuit is stable.
- Taking Laplace transform yields

$$(5.1-2) \quad \hat{y}(s) = \underbrace{\frac{p_2 s^2 + p_1 s + p_0}{s^3 + a_2 s^2 + a_1 s + a_0}}_{\hat{p}(s)} + \underbrace{\frac{b_2 s^2 + b_1 s + b_0}{s^3 + a_2 s^2 + a_1 s + a_0}}_{\hat{h}(s)} \hat{v}(s)$$

where $\hat{v}(s) = \frac{Vs}{s^2 + \omega^2}$, $\hat{p}(s)$ is related to the initial conditions and $\hat{h}(s)$ is the transfer function of the circuit.

- Hence,

$$(5.1-3) \quad y(t) = p(t) + h(t) * v(t) \Rightarrow y(t) = h(t) * v(t), \text{ as } t \rightarrow \infty$$

where $p(\infty) = 0$ because $Re(\lambda_i) < 0$, $i=1,2,3$.

- That means $y(t)|_{t \rightarrow \infty}$ can be solved by

$$(5.1-4) \quad \begin{aligned} \hat{y}(s) &= \hat{h}(s) \frac{Vs}{s^2 + \omega^2} = \frac{b_2 s^2 + b_1 s + b_0}{s^3 + a_2 s^2 + a_1 s + a_0} \cdot \frac{Vs}{s^2 + \omega^2} \\ &= \frac{q_2 s^2 + q_1 s + q_0}{s^3 + a_2 s^2 + a_1 s + a_0} + \frac{As + B\omega}{s^2 + \omega^2} = \hat{q}(s) + \frac{As + B\omega}{s^2 + \omega^2} \end{aligned}$$

which leads to $y(t) = q(t) + A \cos \omega t + B \sin \omega t$. Similarly, $Re(\lambda_i) < 0$, $i=1,2,3$,

results in $q(\infty) = 0$ and

$$(5.1-5) \quad y(t) = A \cos \omega t + B \sin \omega t = Y \cos(\omega t + \theta), \text{ as } t \rightarrow \infty$$

where $Y = \sqrt{A^2 + B^2}$ and $\theta = -\tan^{-1}(B/A)$.

- From (5.1-4), it can be obtained that

$$(5.1-6) \quad \hat{q}(s)(s^2 + \omega^2) + (As + B\omega) = Vs \cdot \hat{h}(s)$$

Let $s = j\omega$, then $s^2 + \omega^2 = 0$ and $(As + B\omega) = Vs \cdot \hat{h}(s)$, i.e.,

$$(5.1-7) \quad (jA\omega + B\omega) = jV\omega \cdot \hat{h}(j\omega)$$

$$\Rightarrow (A - jB) = V \cdot \hat{h}(j\omega) \Rightarrow Ye^{j\theta} = V |\hat{h}(j\omega)| e^{j\angle\hat{h}(j\omega)}$$

where $\hat{h}(j\omega) = |\hat{h}(j\omega)| e^{j\angle\hat{h}(j\omega)}$, $Y = V |\hat{h}(j\omega)|$ and $\theta = \angle\hat{h}(j\omega)$, then

$$(5.1-8) \quad y(t) = V |\hat{h}(j\omega)| \cos(\omega t + \angle\hat{h}(j\omega))$$

- To sum up, if the input of an RLC circuit is $v(t) = V \cos(\omega t)$, then the output is $y(t) = V |\hat{h}(j\omega)| \cos(\omega t + \angle\hat{h}(j\omega))$ which can be solved by using the Laplace transform and setting $s = j\omega$.

5.2 Phasor of sinusoidal signals

- A signal $v(t)$ with a single frequency ω is expressed as

$$(5.2-1) \quad v(t) = V \cos(\omega t + \theta)$$

where V is the magnitude and θ is the phase of the signal.

- Using the Euler formula $e^{j\theta} = \cos \theta + j \sin \theta$ can obtain

$$(5.2-2) \quad v(t) = V \cos(\omega t + \theta) = \operatorname{Re}(V e^{j(\omega t + \theta)}) = \operatorname{Re}(V e^{j\theta} e^{j\omega t}) = \operatorname{Re}(V e^{j\theta} e^{j\omega t})$$

where

$$(5.2-3) \quad V = V e^{j\theta} = V \angle \theta = V \cos \theta + jV \sin \theta$$

and $V = V e^{j\theta}$ is called the phasor of $v(t) = V \cos(\omega t + \theta)$.

Example: If $v(t) = 2 \sin(4t - 30^\circ)$, determine its phasor.

Example: Determine the sinusoidal signal $v(t)$ with frequency $\omega = 3$ and phasor $V = 5 \angle 60^\circ$.

5.3 Components in Phasor Method

- Voltage source $v_s(t) = V_s \cos(\omega t + \theta_s)$


Since $v_s(t) = V_s \cos(\omega t + \theta_s) = \text{Re}(V_s e^{j\theta_s} e^{j\omega t})$, the voltage source in phasor method is

$$(5.3-1) \quad V_s = V_s e^{j\theta_s} = V_s \angle \theta_s$$

- Current source $i_s(t) = I_s \cos(\omega t + \theta_s)$

Since $i_s(t) = I_s \cos(\omega t + \theta_s) = \text{Re}(I_s e^{j\theta_s} e^{j\omega t})$, the current source in phasor method is
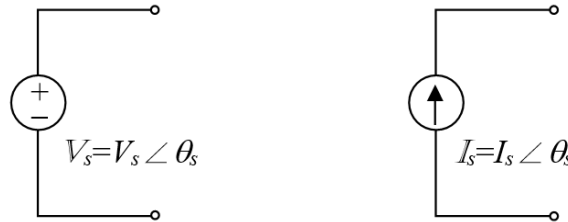
$$(5.3-2) \quad I_s = I_s e^{j\theta_s} = I_s \angle \theta_s$$



- Resistor with component equation $v_R(t) = R \cdot i_R(t)$


If $v_R(t) = V_R \cos \omega t = \text{Re}(V_R e^{j0^\circ} e^{j\omega t})$, then $i_R(t) = I_R \cos \omega t = \text{Re}(I_R e^{j0^\circ} e^{j\omega t})$

where $I_R = \frac{V_R}{R}$. Their phasors are

$$(5.3-3) \quad V_R = V_R e^{j0^\circ} = V_R \angle 0^\circ \quad \text{and} \quad I_R = \frac{V_R}{R} e^{j0^\circ} = I_R \angle 0^\circ.$$

The impedance and admittance (or complex resistance and conductance) of a resistor are respectively defined as
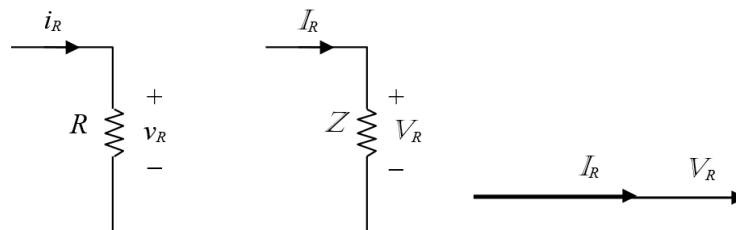
$$(5-3.4) \quad Z_R = \frac{V_R}{I_R} = R \quad (\Omega) \quad \text{and} \quad Y_R = \frac{I_R}{V_R} = \frac{1}{R} \quad (\text{S})$$



- Capacitor with component equation $i_c(t) = C \frac{dv_c(t)}{dt}$

If $v_c(t) = V_c \cos \omega t = \text{Re}(V_c e^{j0^\circ} e^{j\omega t})$, then

$$\begin{aligned} i_c(t) &= -\omega C V_c \sin \omega t = \omega C V_c \cos(\omega t + 90^\circ) \\ &= I_c \cos(\omega t + 90^\circ) = \text{Re}(I_c e^{j90^\circ} e^{j\omega t}) \end{aligned}$$

Their phasors are


$$(5-3.5) \quad V_c = V_c e^{j0^\circ} = V_c \angle 0^\circ \quad \text{and} \quad I_c = \omega C V_c e^{j90^\circ} = I_c \angle 90^\circ.$$

The impedance and admittance of a capacitor are respectively defined as

$$(5-3.6) \quad Z_c = \frac{V_c}{I_c} = \frac{V_c}{\omega C V_c \angle 90^\circ} = \frac{1}{\omega C} \angle (-90^\circ) = \frac{1}{j\omega C} \quad (\Omega)$$

$$(5-3.7) \quad Y_c = \frac{I_c}{V_c} = \omega C \angle 90^\circ = j\omega C \quad (\text{S})$$

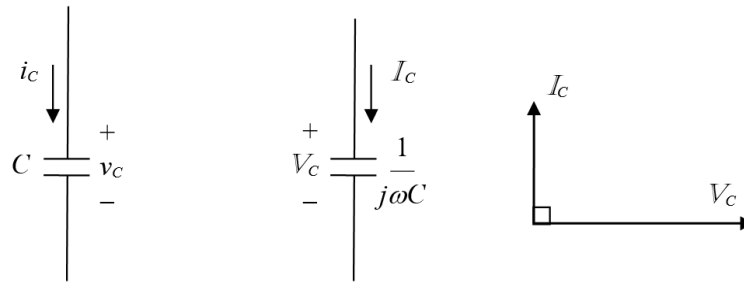Compared to the voltage, the current phasor is leading 90° in phase.



- Inductor with component equation $v_L(t) = L \frac{di_L(t)}{dt}$

If $i_L(t) = I_L \cos \omega t = \text{Re}(I_L e^{j0^\circ} e^{j\omega t})$, then

$$\begin{aligned} v_L(t) &= -\omega L I_L \sin \omega t = \omega L I_L \cos(\omega t + 90^\circ) \\ &= V_L \cos(\omega t + 90^\circ) = \text{Re}(V_L e^{j90^\circ} e^{j\omega t}) \end{aligned}$$

Their phasors are


$$(5.3-8) \quad I_L = I_L e^{j0^\circ} = I_L \angle 0^\circ \quad \text{and} \quad V_L = \omega L I_L e^{j90^\circ} = V_L \angle 90^\circ.$$

The impedance and admittance of an inductor are respectively as

$$(5-3.9) \quad Z_L = \frac{V_L}{I_L} = \frac{\omega L I_L \angle 90^\circ}{I_L} = \omega L \angle 90^\circ = j\omega L \quad (\Omega)$$


$$(5-3.10) \quad Y_L = \frac{I_L}{V_L} = \frac{I_L}{\omega L I_L \angle 90^\circ} = \frac{1}{\omega L} \angle (-90^\circ) = \frac{1}{j\omega L} \quad (\text{S})$$

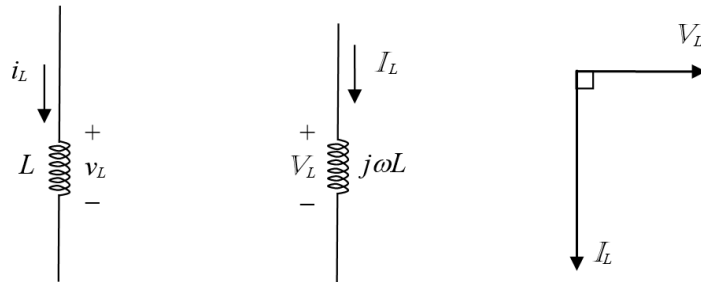Compared to the current, the voltage phasor is leading 90° in phase.



5.4 Circuit Analysis

- Equivalent impedance

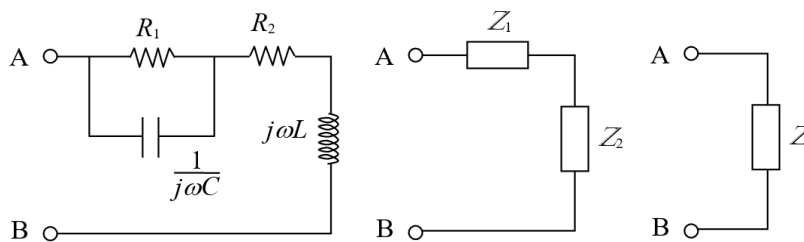

The impedances are $Z_{R1} = R_1$, $Z_{R2} = R_2$, $Z_C = \frac{1}{j\omega C}$ and $Z_L = j\omega L$.

Since R_1 and C are in parallel and R_2 and L are in series, we have


$$(5.4-1) \quad Z_1 = \left(\frac{1}{Z_{R1}} + \frac{1}{Z_C} \right)^{-1} = \left(\frac{1}{R_1} + j\omega C \right)^{-1} = \frac{R_1}{1 + j\omega R_1 C}$$

$$(5.4-2) \quad Z_2 = Z_{R2} + Z_L = R_2 + j\omega L$$


Both Z_1 and Z_2 are in series and result in the equivalent impedance

$$(5.4-3) \quad Z = Z_1 + Z_2 = \frac{R_1}{1 + j\omega R_1 C} + R_2 + j\omega L$$


- Example: $Z = ?$

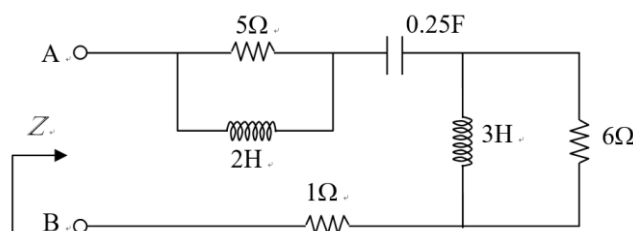


- Example: $v_2(t) = ?$

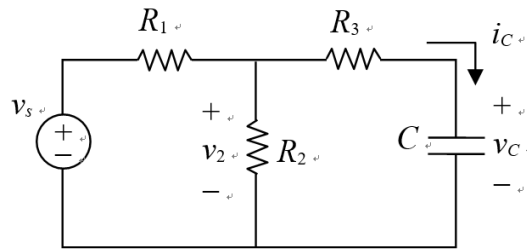

- Example: $v_2(t) = ?$

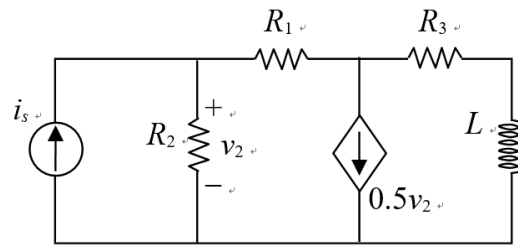


- Example: $i(t) = ?$

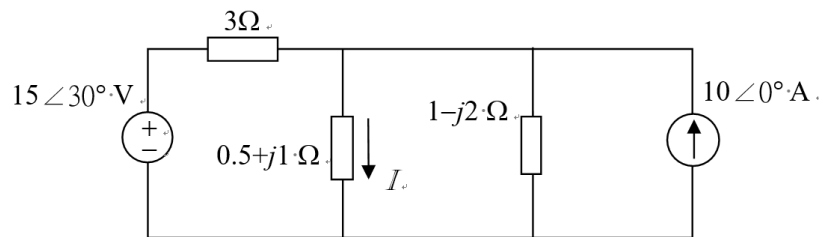

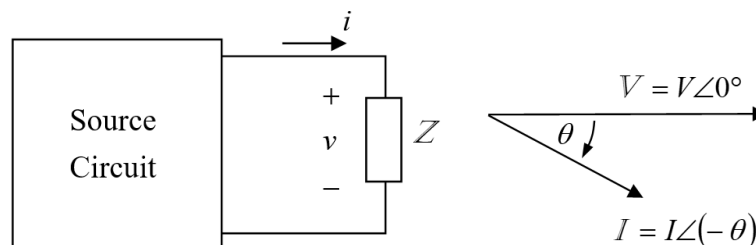5.5 Complex power

- Consider a payload with impedance Z connected to a source circuit, where $v(t) = V \cos \omega t$ and $i(t) = I \cos(\omega t - \theta)$.



The phasors of $v(t) = V \cos \omega t$ and $i(t) = I \cos(\omega t - \theta)$ are $V = V\angle 0^\circ$ and $I = I\angle(-\theta)$. The phase of the current is lagging the voltage by θ .

- The instantaneous power at t absorbed by the payload is

$$\begin{aligned}
 (5.5-1) \quad p(t) &= v(t)i(t) = VI \cos \omega t \cos(\omega t - \theta) \\
 &= \frac{1}{2}VI \cos \theta + \frac{1}{2}VI \cos(2\omega t - \theta) \\
 &= \underbrace{\frac{1}{2}VI \cos \theta}_{P} (1 + \cos 2\omega t) + \underbrace{\frac{1}{2}VI \sin \theta \sin 2\omega t}_{Q} \\
 &= 2P \cos^2 \omega t + Q \sin 2\omega t
 \end{aligned}$$

- The average of power in one period T is

$$\begin{aligned}
 (5.5-2) \quad P_{av} &= \frac{1}{T} \int_T p(t) dt = \frac{2P}{T} \underbrace{\int_T \cos^2 \omega t dt}_{=T/2} + \frac{Q}{T} \underbrace{\int_T \sin 2\omega t dt}_{=0} \\
 &= \frac{2P}{T} \cdot \frac{T}{2} = P = \frac{1}{2}VI \cos \theta
 \end{aligned}$$

Since only P is absorbed in one period, we call P the real power. On the other hand, Q is reserved in the circuit and called the reactive power.

- The root-mean-square(rms) values or effective values of $v(t) = V \cos \omega t$ and $i(t) = I \cos(\omega t - \theta)$ are calculated as

$$(5.5-3) \quad \tilde{V} = \sqrt{\frac{1}{T} \int_T v^2(t) dt} = \sqrt{\frac{V^2}{T} \int_T \cos^2 \omega t dt} = \sqrt{\frac{V^2}{T} \cdot \frac{T}{2}} = \frac{V}{\sqrt{2}}$$

$$(5.5-4) \quad \tilde{I} = \sqrt{\frac{1}{T} \int_T i^2(t) dt} = \sqrt{\frac{I^2}{T} \int_T \cos^2(\omega t - \theta) dt} = \sqrt{\frac{I^2}{T} \cdot \frac{T}{2}} = \frac{I}{\sqrt{2}}$$

- The phasors of $v(t) = V \cos \omega t$ and $i(t) = I \cos(\omega t - \theta)$ are defined as

$$(5.5-5) \quad \tilde{V} = \frac{V}{\sqrt{2}} = \frac{V}{\sqrt{2}} \angle 0^\circ = \tilde{V} \angle 0^\circ$$

$$(5.5-6) \quad \tilde{I} = \frac{I}{\sqrt{2}} = \frac{I}{\sqrt{2}} \angle(-\theta) = \tilde{I} \angle(-\theta)$$


- The complex power is defined as

$$\begin{aligned}
 (5.5-7) \quad S &= \tilde{V} \tilde{I}^* = \tilde{V} \tilde{I} \angle \theta = \frac{V}{\sqrt{2}} \frac{I}{\sqrt{2}} e^{j\theta} \\
 &= \frac{1}{2}VI \cos \theta + j \frac{1}{2}VI \sin \theta = P + jQ = S \angle \theta \quad (\text{VA: volt-ampere})
 \end{aligned}$$

where $S = |S| = \tilde{V} \tilde{I} = \frac{1}{2} VI$ (VA) is called the apparent power. Hence,

$$(5.5-8) \quad P = \frac{1}{2} VI \cos \theta = \operatorname{Re}(\tilde{V} \tilde{I}^*) = \operatorname{Re}(S) = S \cos \theta \quad (\text{W})$$
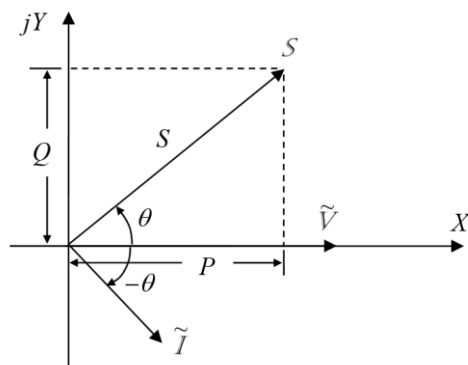
$$(5.5-9) \quad Q = \frac{1}{2} VI \sin \theta = \operatorname{Im}(\tilde{V} \tilde{I}^*) = \operatorname{Im}(S) = S \sin \theta \quad (\text{VAR})$$



- Let $Z = R + jX$ where R is the resistance and X is the reactance.

Since $\tilde{V} = \tilde{I}Z$, we have

$$(5.5-10) \quad Z = \frac{\tilde{V}}{\tilde{I}} = \frac{\tilde{V}}{\tilde{I}} \angle \theta = \frac{V}{I} \angle \theta = Z \angle \theta$$

Therefore, the complex power can be described as

$$(5.5-11) \quad S = \tilde{V} \tilde{I}^* = \tilde{I} \tilde{I}^* Z = \begin{cases} \tilde{I}^2 Z \angle \theta = S \angle \theta \\ \tilde{I}^2 (R + jX) = \tilde{I}^2 R + j \tilde{I}^2 X = P + jQ \end{cases}$$

where

$$(5.5-12) \quad S = \tilde{I}^2 Z = \frac{1}{2} I^2 Z \quad (\text{VA})$$

$$(5.5-13) \quad P = \tilde{I}^2 R = \frac{1}{2} I^2 R \quad (\text{W})$$

$$(5.5-14) \quad Q = \tilde{I}^2 X = \frac{1}{2} I^2 X \quad (\text{VAR})$$

5.6 Conservation of energy

- The conservation of energy implies the total power in a circuit is zero, i.e.,

$$(5.6-1) \quad p(t) = \sum_{k=1}^n p_k(t) = \sum_{k=1}^n v_k(t) i_k(t) = 0$$

Since the power of the k^{th} component is

$$(5.6-2) \quad p_k(t) = 2P_k \cos^2 \omega t + Q_k \sin 2\omega t, \quad k=1,2,\dots,n$$

it can be obtained that

$$(5.6-3) \quad \begin{aligned} \sum_{k=1}^n p_k(t) &= \sum_{k=1}^n (2P_k \cos^2 \omega t + Q_k \sin 2\omega t) \\ &= 2 \left(\sum_{k=1}^n P_k \right) \cos^2 \omega t + \left(\sum_{k=1}^n Q_k \right) \sin 2\omega t = 0 \end{aligned}$$


which leads to $\sum_{k=1}^n P_k = 0$ and $\sum_{k=1}^n Q_k = 0$.

Thus, the total complex power satisfies

$$(5.6-4) \quad S = \sum_{k=1}^n S_k = \sum_{k=1}^n P_k + j \sum_{k=1}^n Q_k = 0$$

In other words, the conservation of energy also implies the total complex power is equal to zero.

5.7 The maximum power transfer theorem

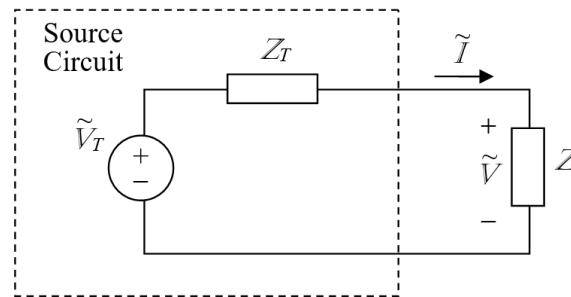

- Assume $\tilde{V}_T = \tilde{V}_T \angle 0^\circ$, $Z_T = R_T + jX_T$ and $Z = R + jX$, then

$$(5.7-1) \quad \tilde{V} = \frac{Z}{Z_T + Z} \tilde{V}_T \quad \text{and} \quad \tilde{I} = \frac{\tilde{V}_T}{Z_T + Z}$$

The complex power of payload is

$$(5.7-2) \quad \begin{aligned} \tilde{V}\tilde{I}^* &= \frac{Z}{(Z_T + Z)(Z_T^* + Z^*)} \tilde{V}_T \tilde{V}_T^* \\ &= \frac{R + jX}{(R_T + R)^2 + (X_T + X)^2} \tilde{V}_T^2 = P + jQ \end{aligned}$$

- The real power transferred to the payload is

$$(5.7-3) \quad P = \operatorname{Re}(\tilde{V}\tilde{I}^*) = \frac{R\tilde{V}_T^2}{(R_T + R)^2 + (X_T + X)^2}$$

- The maximum real power can be obtained when $\frac{\partial P}{\partial R} = 0$ and $\frac{\partial P}{\partial X} = 0$, i.e.,

$$(5.7-4) \quad \frac{\partial P}{\partial X} = \frac{-2R(X_T + X)}{\left((R_T + R)^2 + (X_T + X)^2\right)^2} \tilde{V}_T^2 = 0 \Rightarrow X = -X_T$$

$$(5.7-5) \quad \frac{\partial P}{\partial R} = \frac{R_T^2 - R^2 + (X_T + X)^2}{\left((R_T + R)^2 + (X_T + X)^2\right)^2} \tilde{V}_T^2 = 0 \Rightarrow R = R_T$$

which results in $Z = R_T - jX_T = Z_T^*$, called the matching impedance.

- When $Z = Z_T^*$, the source circuit generates the real power

$$(5.7-6) \quad P_T = \operatorname{Re}(\tilde{V}_T \tilde{I}^*) = \operatorname{Re}\left(\tilde{V}_T \left(\frac{\tilde{V}_T}{Z_T + Z}\right)^*\right) = \frac{\tilde{V}_T^2}{2R_T}$$

and the payload absorbs the maximum real power

$$(5.7-7) \quad P_{max} = \operatorname{Re}(\tilde{V}\tilde{I}^*) = \frac{\tilde{V}_T^2}{4R_T} = \frac{1}{2} P_T$$

That means the maximum real power can be transferred to the payload is only half of the real power generated by the source circuit.

- Consider a special case that the payload is a real resistance, i.e., $Z = R$.

Then, the real power transferred to the payload is

$$(5.7-8) \quad P = \operatorname{Re}(\tilde{V}\tilde{I}^*) = \frac{R}{(R_T + R)^2 + X_T^2} \tilde{V}_T^2$$

The maximum real power can be obtained when $\frac{\partial P}{\partial R} = 0$, i.e.,

$$(5.7-9) \quad \frac{\partial P}{\partial R} = \frac{R_T^2 + X_T^2 - R^2}{\left((R_T + R)^2 + X_T^2\right)^2} \tilde{V}_T^2 = 0 \Rightarrow R = \sqrt{R_T^2 + X_T^2}$$

- When $R = \sqrt{R_T^2 + X_T^2}$, the source circuit generates the real power

$$\begin{aligned}
 (5.7-10) \quad P_T &= \operatorname{Re}(\tilde{V}_T \tilde{I}^*) = \operatorname{Re}\left(\tilde{V}_T \left(\frac{\tilde{V}_T}{Z_T + R}\right)^*\right) = \operatorname{Re}\left(\frac{\tilde{V}_T^2}{R + R_T - jX_T}\right) \\
 &= \frac{\tilde{V}_T^2 (R + R_T)}{(R + R_T)^2 + X_T^2} = \frac{\tilde{V}_T^2 (R + R_T)}{R^2 + 2RR_T + R_T^2 + X_T^2} = \frac{\tilde{V}_T^2 (R + R_T)}{2R^2 + 2RR_T} = \frac{\tilde{V}_T^2}{2R}
 \end{aligned}$$

and the payload absorbs the maximum real power

$$\begin{aligned}
 (5.7-11) \quad P_{max} &= \operatorname{Re}(\tilde{V} \tilde{I}^*) = \operatorname{Re}\left(\frac{\tilde{V} \tilde{V}^*}{R}\right) = \frac{\tilde{V} \tilde{V}^*}{R} \\
 &= \frac{R \tilde{V}_T \tilde{V}_T^*}{(Z_T + R)(Z_T^* + R)} = \frac{\tilde{V}_T^2}{2(R + R_T)} = \frac{R}{R + R_T} P_T
 \end{aligned}$$

Hence, the maximum real power can be transferred to the payload is $\frac{R}{R + R_T}$


times of the real power generated by the source circuit.

- Example:

Assume the voltage source is $\tilde{V}_s = 110 \angle 0^\circ$ V.


(A) Determine the maximum real power P_{max} transferred to $Z = R + jX$.

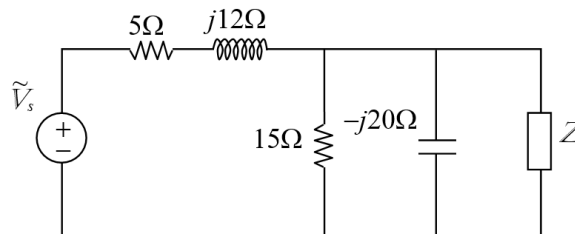(B) Determine the maximum real power P_{max} transferred to $Z = R$.



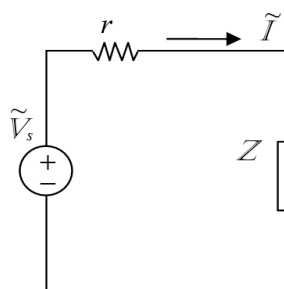5.8 Power factor correction

- The electric power transmitted from \tilde{V}_s to the inductive payload $Z = R + jX$ with $X > 0$, and assume r is a small resistance of the transmission line.



- If $\tilde{V}_s = \tilde{V}_s \angle 0^\circ$, then the current is

$$(5.8-1) \quad \tilde{I} = \frac{\tilde{V}_s}{r+Z} = \frac{\tilde{V}_s}{r+R+jX}$$

and the complex power transferred to the payload is

$$(5.8-2) \quad S_z = Z\tilde{I}\tilde{I}^* = \frac{(R+jX)\tilde{V}_s\tilde{V}_s^*}{(r+R)^2+X^2} = \frac{(R+jX)\tilde{V}_s^2}{(r+R)^2+X^2}$$

$$= \underbrace{\frac{R\tilde{V}_s^2}{(r+R)^2+X^2}}_P + j \underbrace{\frac{X\tilde{V}_s^2}{(r+R)^2+X^2}}_Q$$

$$= S_z \angle \theta = S_z \cos \theta + jS_z \sin \theta$$

- Define the power factor of Z as

$$(5.8-3) \quad pf = \cos \theta = \frac{P}{S_z} = \frac{R}{\sqrt{R^2+X^2}}$$

In other words, the power factor is the ratio of real power to the apparent power.


That implies the power factor will be increased if the reactance X is reduced.

- The power dissipated by the resistance r is

$$(5.8-4) \quad P_r = r\tilde{I}\tilde{I}^* = \frac{r\tilde{V}_s\tilde{V}_s^*}{(r+R)^2+X^2} = \frac{r\tilde{V}_s^2}{(r+R)^2+X^2}$$

which implies P_r will be decreased if the reactance X is reduced.

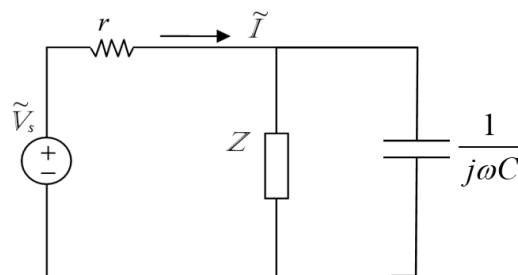- Power factor correction of inductive payload can be achieved by connecting a capacitor parallel to the payload, depicted as below:



Since $Y = Z^{-1} = \frac{1}{R+jX} = \frac{R}{R^2+X^2} - j\frac{X}{R^2+X^2}$, the new payload is

$$(5.8-5) \quad Y_{new} = Y \parallel j\omega C = \frac{R}{R^2+X^2} - j\frac{X}{R^2+X^2} + j\omega C$$

If $C = \frac{X}{\omega(R^2 + X^2)}$, then $Y_{new} = \frac{R}{R^2 + X^2}$, i.e.,

$$(5.8-6) \quad Z_{new} = R + \frac{X^2}{R}$$

Hence, the power dissipated by the resistance r is obtained as

$$(5.8-7) \quad P_r = r \tilde{I} \tilde{I}^* = \frac{r \tilde{V}_s \tilde{V}_s^*}{\left(r + R + \frac{X^2}{R}\right)^2} = \frac{r \tilde{V}_s^2}{\left(r + R + \frac{X^2}{R}\right)^2}$$

$$= \frac{r \tilde{V}_s^2}{(r + R)^2 + 2\left(1 + \frac{r}{R}\right)X^2 + \frac{X^4}{R^2}} < \frac{r \tilde{V}_s^2}{(r + R)^2 + X^2}$$

It is clear that the power P_r is indeed reduced after power factor correction.