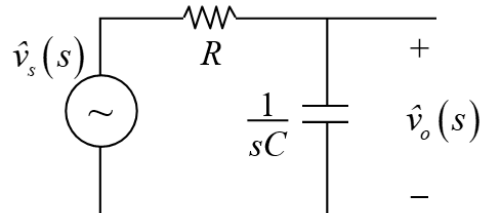


Chap 6 Linear Circuits with Operational Amplifier

6.1 Fundamental concepts of filters

- First-order low pass-filter implemented by an RC circuit:



- Assume the voltage source is

$$(6.1-1) \quad v_s(t) = V_s \cos(\omega t) \quad \text{or} \quad \hat{v}_s(s) = V_s \frac{s}{s^2 + \omega^2}.$$

Then, the output voltage is

$$(6.1-2) \quad \hat{v}_o(s) = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} \hat{v}_s(s) = \frac{1}{\underbrace{1 + sRC}_{H(s)}} \cdot \hat{v}_s(s) = H(s) \frac{V_s s}{s^2 + \omega^2}$$

- As $t \rightarrow \infty$, let $s = j\omega$ and obtain $H(j\omega) = \frac{1}{1 + j\omega RC}$, or expressed as


$$(6.1-3) \quad H(j\omega) = |H(j\omega)| e^{j\angle H(j\omega)} = \frac{1}{\sqrt{1 + (\omega RC)^2}} e^{j\theta}$$

where $|H(j\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$ and $\theta = \angle H(j\omega) = -\tan^{-1}(\omega RC)$.

- If $v_s(t) = V_s \cos(\omega t)$ then the output voltage is

$$(6.1-4) \quad v_o(t) = |H(j\omega)| V_s \cos(\omega t + \theta) = V_0 \cos(\omega t + \theta)$$


where $V_0 = |H(j\omega)| V_s$.

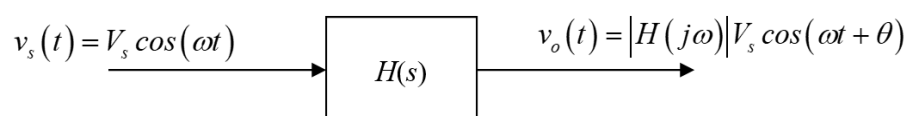


- It is easy to check that $|H(j\omega)| = \frac{1}{\sqrt{1+(\omega RC)^2}} < 1$, i.e., $V_o < V_s$ and

$$(6.1-5) \quad |H(j\omega)| = \begin{cases} 1^- & \omega \rightarrow 0 \\ 1/\sqrt{2} & \omega = \omega_0 = 1/RC \\ 0^+ & \omega \rightarrow \infty \end{cases}$$

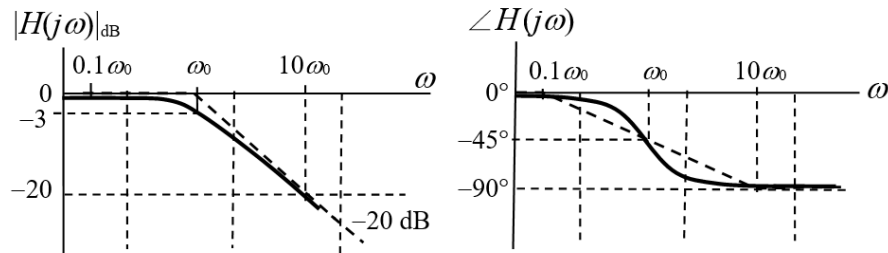The output voltage will be decreased while ω is increased.



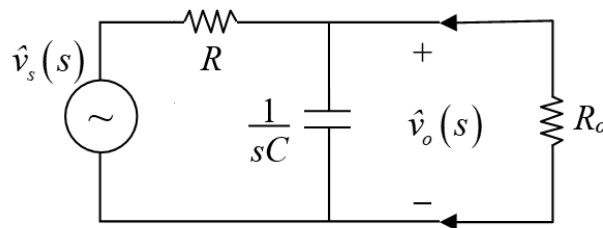- To achieve the output voltage, we often connect a receiver with equivalent resistance R_o , shown as below:



Then, the output voltage is changed as $\hat{v}_o(s) = H_{R_o}(s) \hat{v}_s(s)$ or

$$(6.1-6) \quad \hat{v}_o(s) = \frac{\frac{1}{sC} // R_o}{R + \frac{1}{sC} // R_o} \hat{v}_s(s) = \underbrace{\frac{r}{r(sRC) + 1}}_{H_{R_o}(s)} \cdot \frac{V_s s}{s^2 + \omega^2}$$

where $r = \frac{R_o}{R + R_o} < 1$.

- It is easy to check that $|H_{R_o}(j\omega)| = \frac{r}{\sqrt{1+r^2(\omega RC)^2}} < 1$, i.e., $V_o < V_s$ and



$$(6.1-7) \quad |H_{R_o}(j\omega)| = \begin{cases} r^- & \omega \rightarrow 0 \\ r/\sqrt{2} & \omega = \omega_0 = 1/rRC \\ 0^+ & \omega \rightarrow \infty \end{cases}$$

- Note that if $R_o \rightarrow \infty$, then $r \rightarrow 1$ and $H_{R_o}(j\omega) \approx H(j\omega)$.

However, it is impossible to use $R_o \rightarrow \infty$ since the current through R_o will be very small, so is the output power.

6.2 Ideal Operational Amplifier (OPamp)


- Voltage Amplifier using transistor

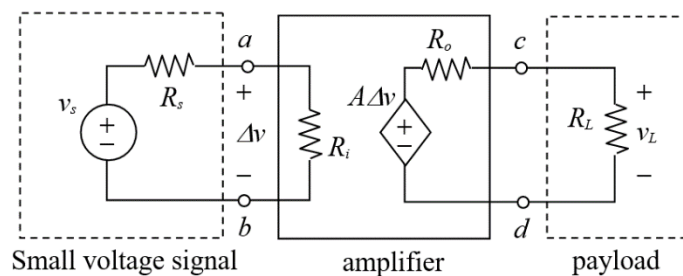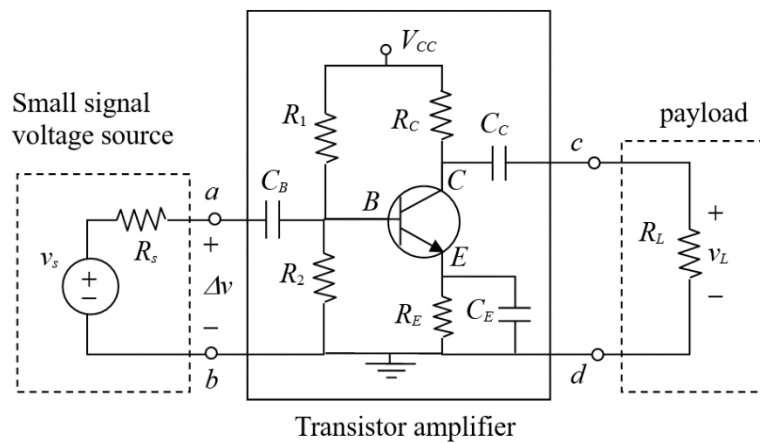


$$(6.2-1) \quad v_L(t) = \frac{R_L}{R_o + R_L} A \Delta v(t) = \left(\frac{R_L}{R_o + R_L} \right) \left(\frac{R_i}{R_i + R_s} \right) A v_s(t)$$

If $R_i \rightarrow \infty$ and $R_o \approx 0$, then $v_L(t) = A v_s(t)$, not affected by R_s and R_L .

- OPamp

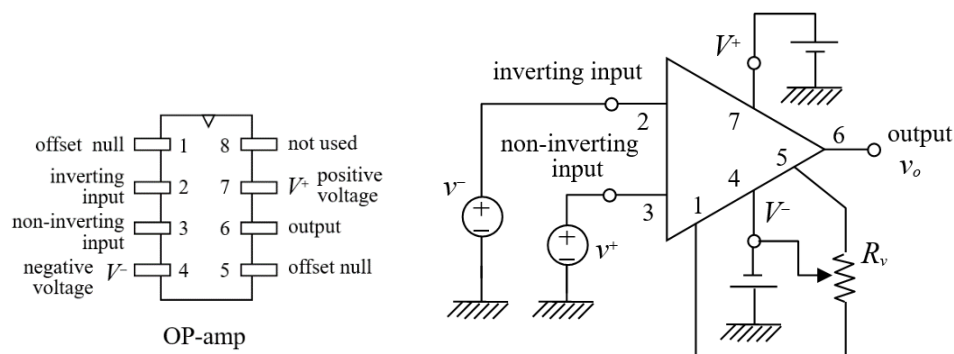

- Important properties

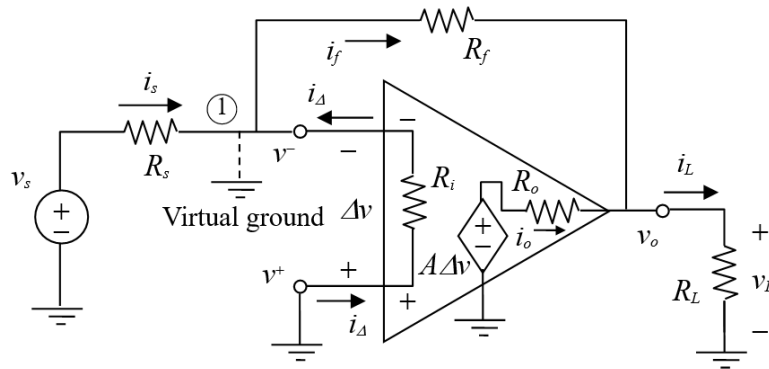


$$(6.2-2) \quad R_i \rightarrow \infty, \quad R_o \approx 0, \quad A \rightarrow \infty,$$


$$(6.2-3) \quad v_o(t) = A \Delta v(t)$$

It implies $\Delta v(t) \approx 0$ and $i_\Delta(t) \rightarrow 0$.

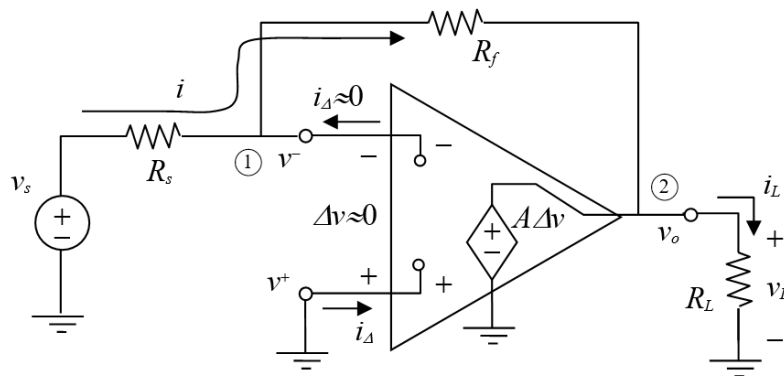In general, we say that the node ① is a virtual ground.




- Equivalent circuit

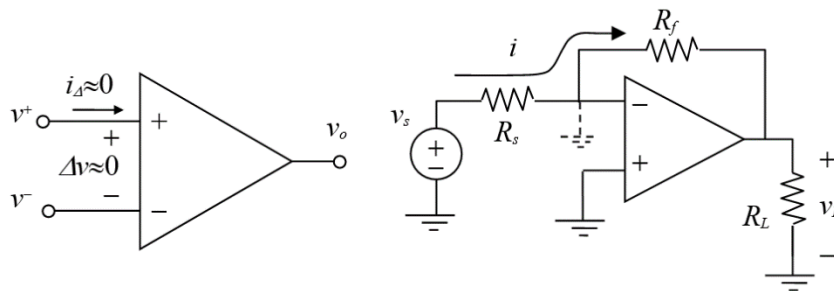

$$(6.2-4) \quad i(t) = \frac{v_s(t)}{R_s} = -\frac{v_L(t)}{R_f} \Rightarrow v_L(t) = -\frac{R_f}{R_s} v_s(t)$$

That means the gain $-\frac{R_f}{R_s}$ is independent to the payload R_L .

- Inverting amplifier

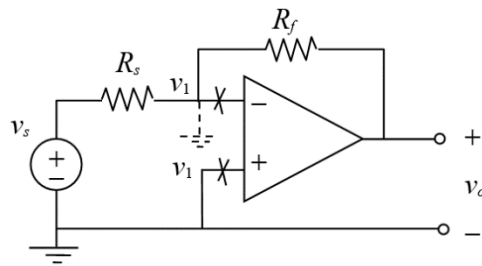


$$(6.2-5) \quad \frac{v_1(t) - v_s(t)}{R_s} + \frac{v_1(t) - v_o(t)}{R_f} = 0 \Rightarrow v_o(t) = -\frac{R_f}{R_s} v_s(t)$$


$$(6.2-6) \quad A_v = \frac{v_o(t)}{v_s(t)} = -\frac{R_f}{R_s}$$

The voltage gain is negative and called the inverting amplifier.

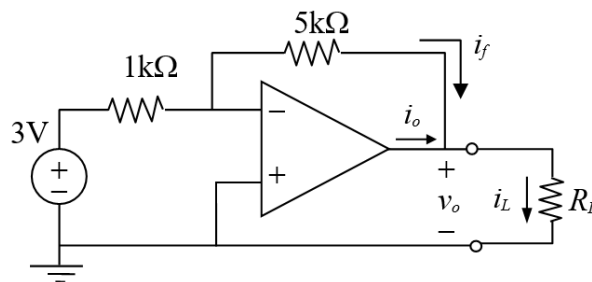Example: If $R_L = 1 \text{ k}\Omega$, what is $i_L(t)$?



- Non-inverting amplifier

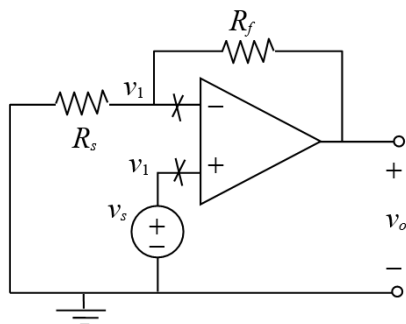


$$(6.2-7) \quad \frac{v_1(t)}{R_s} + \frac{v_1(t) - v_o(t)}{R_f} = 0 \Rightarrow v_o(t) = \left(1 + \frac{R_f}{R_s}\right) v_s(t)$$

$$(6.2-8) \quad A_v = \frac{v_o(t)}{v_s(t)} = 1 + \frac{R_f}{R_s} \geq 1$$


The voltage gain is positive and called the non-inverting amplifier.

It can be used as a buffer, $v_o(t) = v_s(t)$, by setting $R_f=0$ or $R_s=\infty$.

Example: Determine $v_o(t)$.

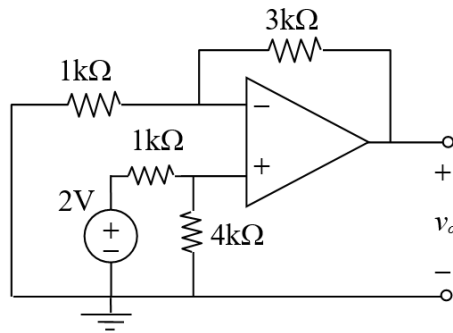

- Addition

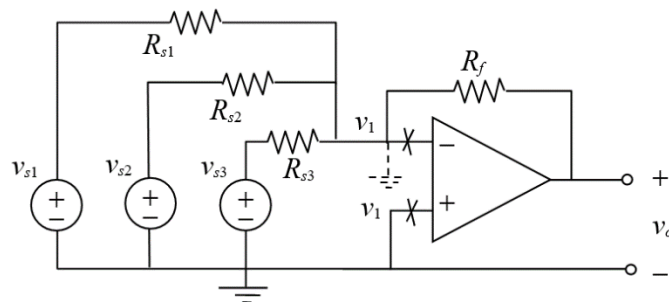


$$(6.2-9) \quad \frac{v_1(t) - v_{s1}(t)}{R_{s1}} + \frac{v_1(t) - v_{s2}(t)}{R_{s2}} + \frac{v_1(t) - v_{s3}(t)}{R_{s3}} + \frac{v_1(t) - v_o(t)}{R_f} = 0$$

$$(6.2-10) \quad v_o(t) = -\left(\frac{R_f}{R_{s1}} v_{s1}(t) + \frac{R_f}{R_{s2}} v_{s2}(t) + \frac{R_f}{R_{s3}} v_{s3}(t) \right)$$

It is an inverting addition.


- Subtraction

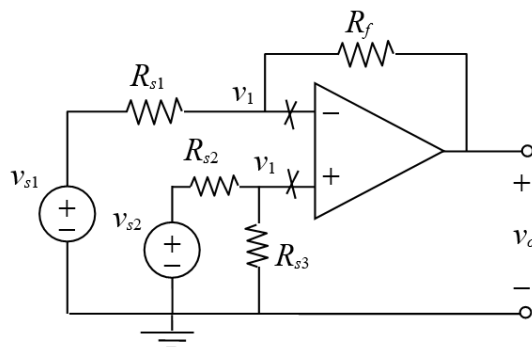

$$(6.2-11) \quad \frac{v_1(t) - v_{s1}(t)}{R_{s1}} + \frac{v_1(t) - v_o(t)}{R_f} = 0, \quad v_1(t) = \frac{R_{s3}}{R_{s2} + R_{s3}} v_{s2}(t)$$

$$(6.2-12) \quad v_o(t) = \frac{R_{s3}(R_f + R_{s1})}{R_{s1}(R_{s3} + R_{s2})} v_{s2}(t) - \frac{R_f}{R_{s1}} v_{s1}(t)$$

- Integrator

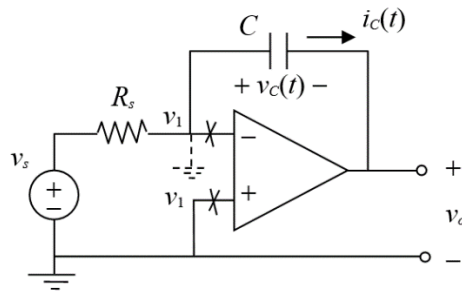

$$(6.2-13) \quad i_c(t) = C \frac{dv_c(t)}{dt} = C \frac{d}{dt}(v_1(t) - v_o(t))$$

$$(6.2-14) \quad \frac{v_1(t) - v_s(t)}{R_s} + i_c(t) = \frac{v_1(t) - v_s(t)}{R_s} + C \frac{d}{dt}(v_1(t) - v_o(t)) = 0$$

Since $v_1(t)=0$, we have


$$(6.2-15) \quad \frac{dv_o(t)}{dt} = -\frac{v_s(t)}{R_s C}$$

$$(6.2-16) \quad v_o(t) = -\frac{1}{R_s C} \int_0^t v_s(\tau) d\tau + v_o(0)$$


It is an inverting integrator.

6.3 RLC circuits with OPAMps


- Example-1

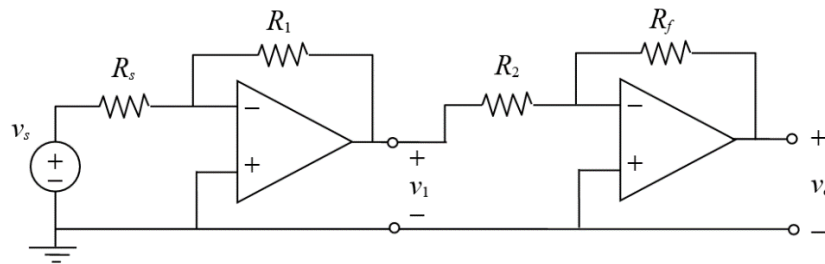


- Example-2

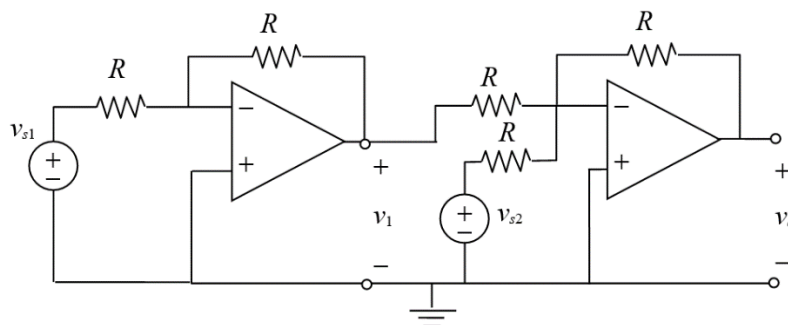


- Example-3

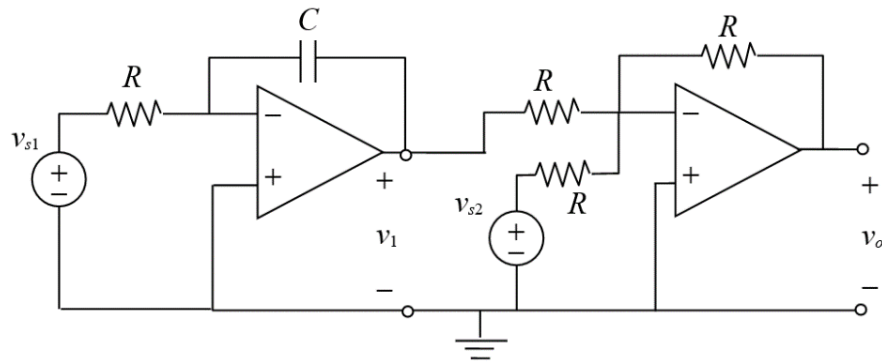


- Example-4

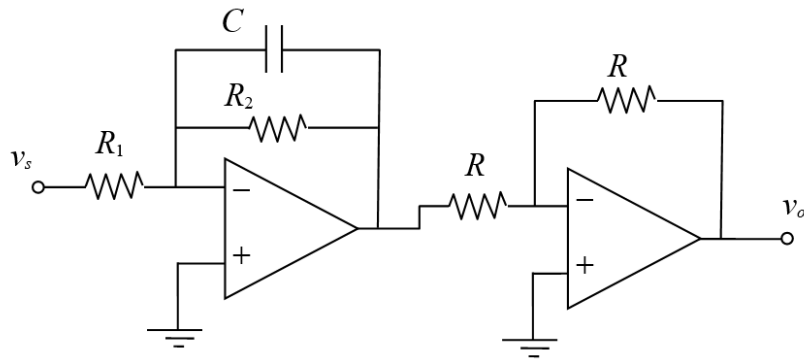


- Example-5

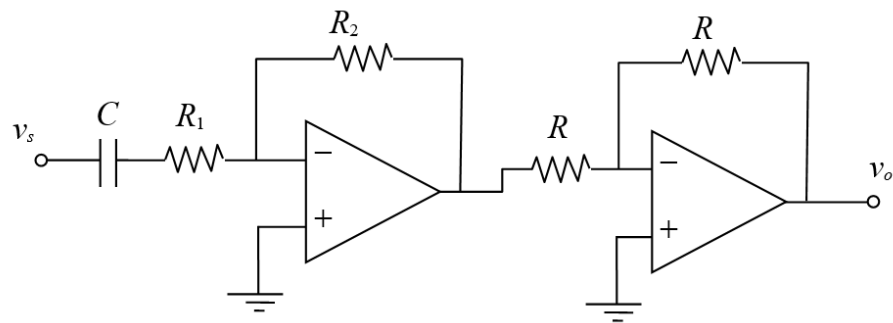

- Example-6

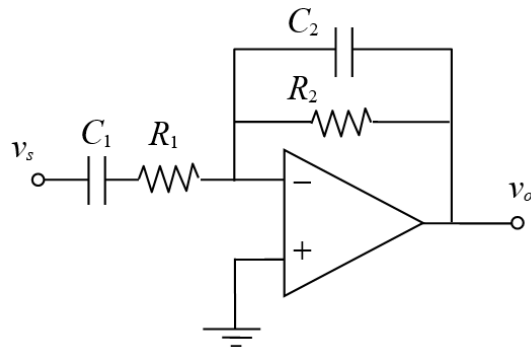

- Example-7

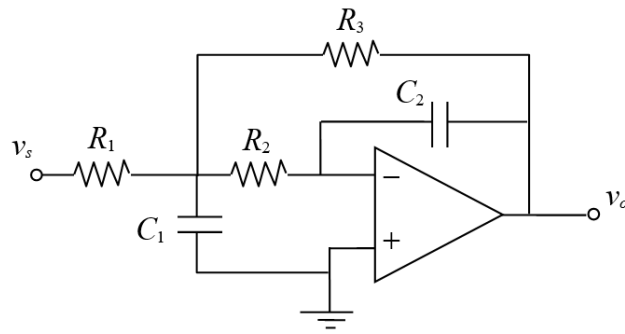

- Example-8

